 


FET Amplifiers

- Excellent voltage gain
- High input impedance
- Low-power consumption
- Good frequency range

Chapter 7: FET Biasing



Step 1: DC analysis Based on DC network:

- V_{GSQ}
- I_{DQ}
- V_{DSQ}

Using V_{GSQ} to determine g_m for AC equivalent model



Chapter 8: FET Amplifiers



- ### Step 2: AC analysis
- Based on AC network and AC equivalent model:
- Input impedance
 - Output impedance
 - Voltage gain

Three basic configurations for FET amplifiers

CS: Common Source Configuration

CG: Common Gate Configuration

Source Follower: Common Drain

Common FET Biasing Circuits

JFET

- Fixed-Bias
- Self-Bias
- Voltage-Divider Bias

Depletion-Type MOSFET

- Self-Bias
- Voltage-Divider Bias

Enhancement-Type MOSFET

- Feedback Configuration
- Voltage-Divider Bias

DC analysis methods: V_{GSQ} , I_{DQ} , V_{DSQ}

- Mathematical approach
- Graphical approach

General Relationships

For all FETs:

$$I_G \cong 0A$$

$$I_D = I_S$$

For JFETs and depletion-type MOSFETs:

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

For enhancement-type MOSFETs:

$$I_D = k(V_{GS} - V_T)^2$$

7.2 Fixed-Bias Configuration

Mathematical Approach




$$I_G \cong 0A$$

$$V_{GSQ} = -V_{GG}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \rightarrow I_{DQ}$$

$$V_{DS} = V_{DD} - I_D R_D \rightarrow V_{DSQ}$$

Graphical Approach

   

7.3 Self-Bias Configuration

Mathematical Approach




$$I_G \cong 0A, \quad I_D = I_S$$

$$V_{GS} = -I_D R_S$$

$$\left. \begin{aligned} V_{GS} &= -I_D R_S \\ I_D &= I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \end{aligned} \right\} \Rightarrow V_{GSQ}, I_{DQ}$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S) \rightarrow V_{DSQ}$$

Graphical Approach

   

7.4 Voltage-Divider Biasing

Mathematical Approach




$$I_G \cong 0\text{A}, \quad I_D = I_S$$

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

$$\left. \begin{aligned} V_{GS} &= V_G - I_D R_S \\ I_D &= I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \end{aligned} \right\} \Rightarrow V_{GSQ}, I_{DQ}$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S) \rightarrow V_{DSQ}$$

Graphical Approach

   

7.6 Feedback Biasing for E-MOSFETs


Mathematical Approach

$$I_G \cong 0A, \quad V_D = V_G$$



$$V_{GS} = V_{DS}$$

$$\left. \begin{aligned} V_{GS} &= V_{DD} - I_D R_D \\ I_D &= k(V_{GS} - V_{GS(TH)})^2 \end{aligned} \right\} \Rightarrow V_{GSQ}, I_{DQ}$$
 
$$V_{DS} = V_{DD} - I_D R_D \rightarrow V_{DSQ}$$



Graphical Approach

  

8.2 FET Small-Signal Model

Transconductance

The relationship of $V_{GS(\text{input})}$ to $I_{D(\text{output})}$ is called **transconductance** denoted by g_m .

Mathematical Determinations of g_m

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$

$$g_m = \frac{2I_{DSS}}{|V_P|} \left[1 - \frac{V_{GS}}{V_P} \right]$$


Where $V_{GS} = 0V$ $g_{m0} = \frac{2I_{DSS}}{|V_P|}$

$$g_m = g_{m0} \left[1 - \frac{V_{GS}}{V_P} \right]$$

Where $1 - \frac{V_{GS}}{V_P} = \sqrt{\frac{I_D}{I_{DSS}}}$

$$g_m = g_{m0} \left(1 - \frac{V_{GS}}{V_P} \right) = g_{m0} \sqrt{\frac{I_D}{I_{DSS}}}$$

Graphical Determination of g_m

 

With a small signal input, FET acts as a linear device: $I_d = g_m V_{gs}$

FET Impedance

Input impedance:

$$Z_i = \infty \Omega$$

Output Impedance:



$$Z_o = r_d = \frac{1}{y_{os}}$$

where:

$$r_d = \left. \frac{\Delta V_{DS}}{\Delta I_D} \right|_{V_{GS} = \text{constant}}$$

y_{os} = admittance equivalent circuit parameter listed on FET specification sheets.

FET AC Equivalent Circuit

  

8.3 JFET Common-Source (CS) Fixed-Bias Configuration

The input is on the gate and the output is on the drain

Input impedance:

$$Z_i = R_G$$

Output impedance:



$$Z_o = R_D \parallel r_d$$

$$Z_o \cong R_D \quad \left| \quad r_d \geq 10R_D \right.$$

Voltage gain:

$$A_v = \frac{V_o}{V_i} = -g_m (r_d \parallel R_D)$$

$$A_v = \frac{V_o}{V_i} = -g_m R_D \quad \left| \quad r_d \geq 10R_D \right.$$

  

CS: There is a 180° phase shift between input and output

8.4 JFET Common-Source Self-Bias Configuration

The input is on the gate and the output is on the drain

Input impedance:

$$Z_i = R_G$$

Output impedance:



$$Z_o = r_d \parallel R_D$$

$$Z_o \cong R_D \Big|_{r_d \geq 10R_D}$$

Voltage gain:

$$A_v = -g_m (r_d \parallel R_D)$$

$$A_v = -g_m R_D \Big|_{r_d \geq 10R_D}$$

  

JFET Common-Source Self-Bias Configuration

Removing C_s affects the gain of the circuit.

Input impedance:

$$Z_i = R_G$$



Output impedance:

$$Z_o \cong R_D \Big|_{r_d \geq 10R_D}$$

Voltage gain:

$$A_v = \frac{V_o}{V_i} = - \frac{g_m R_D}{1 + g_m R_S + \frac{R_D + R_S}{r_d}}$$

$$A_v = \frac{V_o}{V_i} = - \frac{g_m R_D}{1 + g_m R_S} \Big|_{r_d \geq 10(R_D + R_S)}$$

 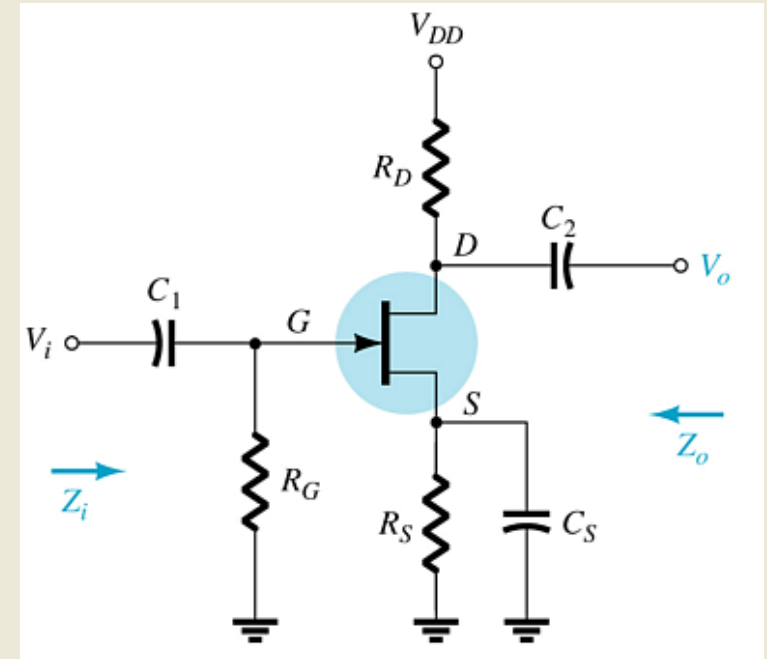

8.5 JFET CS Voltage-Divider Configuration

The input is on the gate and the output is on the drain.

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

$$V_{GS} = V_G - I_D R_S$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

Input impedance:

$$Z_i = R_1 \parallel R_2$$

Output impedance:




$$Z_o = r_d \parallel R_D$$

$$Z_o \cong R_D \quad \left| \quad r_d \geq 10R_D \right.$$

Voltage gain:

$$A_v = -g_m (r_d \parallel R_D)$$

$$A_v = -g_m R_D \quad \left| \quad r_d \geq 10R_D \right.$$

  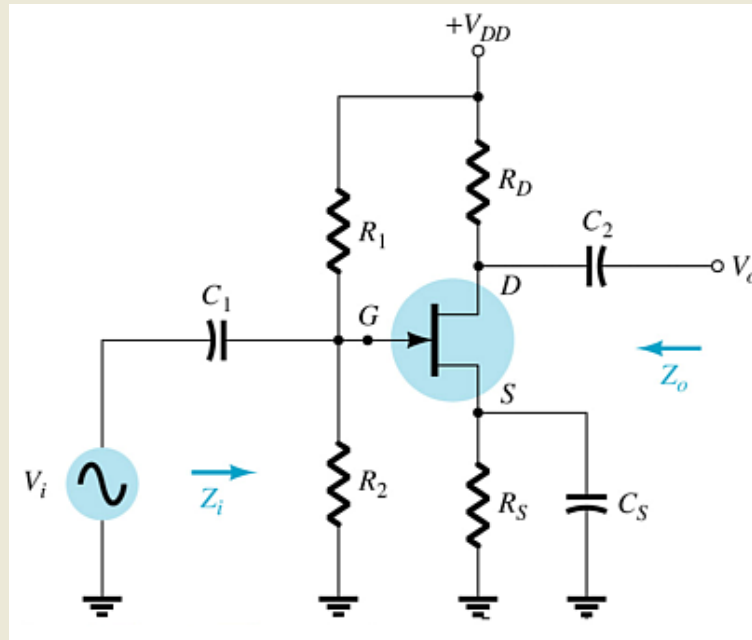

8.6 JFET Source Follower (Common-Drain) Configuration

In a common-drain amplifier configuration, the input is on the gate, but the output is from the source.

There is no phase shift between input and output.

Input impedance:

$$Z_i = R_G$$

Output impedance:



$$Z_o = r_d \parallel R_S \parallel \frac{1}{g_m}$$

$$Z_o \cong R_S \parallel \frac{1}{g_m} \Big|_{r_d \geq 10R_S}$$

Voltage gain:

$$A_v = \frac{V_o}{V_i} = \frac{g_m (r_d \parallel R_S)}{1 + g_m (r_d \parallel R_S)}$$

$$A_v = \frac{V_o}{V_i} = \frac{g_m R_S}{1 + g_m R_S} \Big|_{r_d \geq 10R_S}$$

 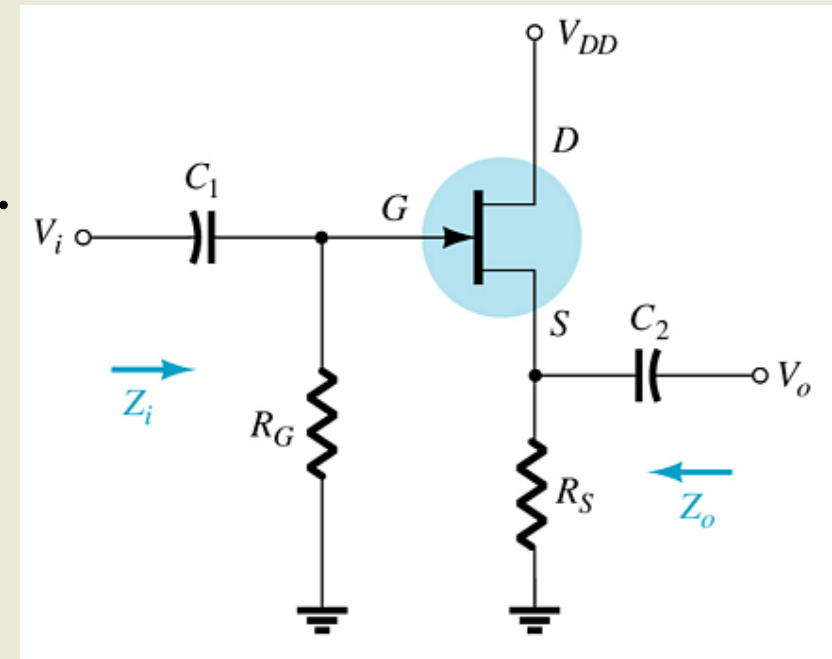

8.7 JFET Common-Gate Configuration

The input is on the source and the output is on the drain.

Input impedance:

$$Z_i = R_S \parallel \left[\frac{r_d + R_D}{1 + g_m r_d} \right]$$

$$Z_i \cong R_S \parallel \frac{1}{g_m} \Big|_{r_d \geq 10R_D}$$

Output impedance:



$$Z_o = R_D \parallel r_d$$

$$Z_o \cong R_D \Big|_{r_d \geq 10R_D}$$

Voltage gain:

$$A_v = \frac{V_o}{V_i} = \frac{\left[g_m R_D + \frac{R_D}{r_d} \right]}{\left[1 + \frac{R_D}{r_d} \right]}$$


$$A_v = g_m R_D \Big|_{r_d \geq 10R_D}$$

  

There is no phase shift between input and output.

 8.8 Depletion-Type MOSFETs

- D-MOSFETs have the same AC equivalent model and same equation for g_m with JFETs .
- The only difference is that V_{GSQ} can be positive for n -channel devices and negative for p -channel devices. This means that g_m can be greater than g_{m0} .



8.9 Enhancement-Type MOSFETs


- E-MOSFETs have the similar AC equivalent model with JFETs .
- Equation for g_m is different.

Transfer equation for E-MOSFETs:

$$I_D = k(V_{GS} - V_T)^2$$

$$g_m = \left. \frac{\Delta I_D}{\Delta V_{GS}} \right|_Q$$

$$g_m = 2k(V_{GSQ} - V_{GS(Th)})$$

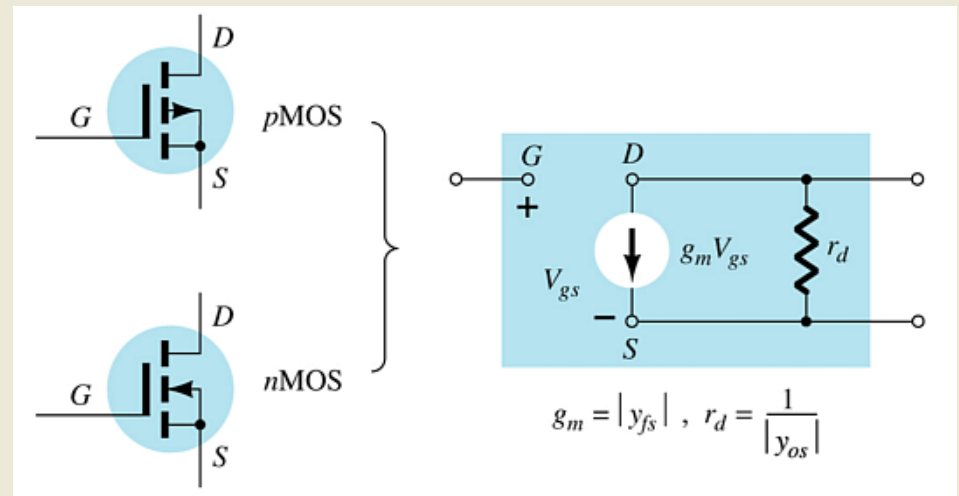

8.10 E-MOSFET CS Drain-Feedback Configuration

There is a 180° phase shift between input and output for CS amplifiers.

Input impedance:

$$Z_i = \frac{R_F + r_d \parallel R_D}{1 + g_m(r_d \parallel R_D)}$$

$$Z_i \cong \frac{R_F}{1 + g_m R_D} \Big|_{R_F \gg r_d \parallel R_D, r_d \geq 10R_D}$$

Output impedance:



$$Z_o = R_F \parallel r_d \parallel R_D$$

$$Z_o \cong R_D \Big|_{R_F \gg r_d \parallel R_D, r_d \geq 10R_D}$$

Voltage gain:

$$A_v = -g_m(R_F \parallel r_d \parallel R_D)$$

$$A_v \cong -g_m R_D \Big|_{R_F \gg r_d \parallel R_D, r_d \geq 10R_D}$$

  

8.11 E-MOSFET CS Voltage-Divider Configuration

Input impedance:

$$Z_i = R_1 \parallel R_2$$

Output impedance:



$$Z_o = r_d \parallel R_D$$

$$Z_o \cong R_D \big|_{r_d \geq 10R_D}$$

Voltage gain:

$$A_v = -g_m (r_d \parallel R_D)$$


$$A_v \cong -g_m R_D \big|_{r_d \geq 10R_D}$$

  

8.13 Effect of R_L and R_S

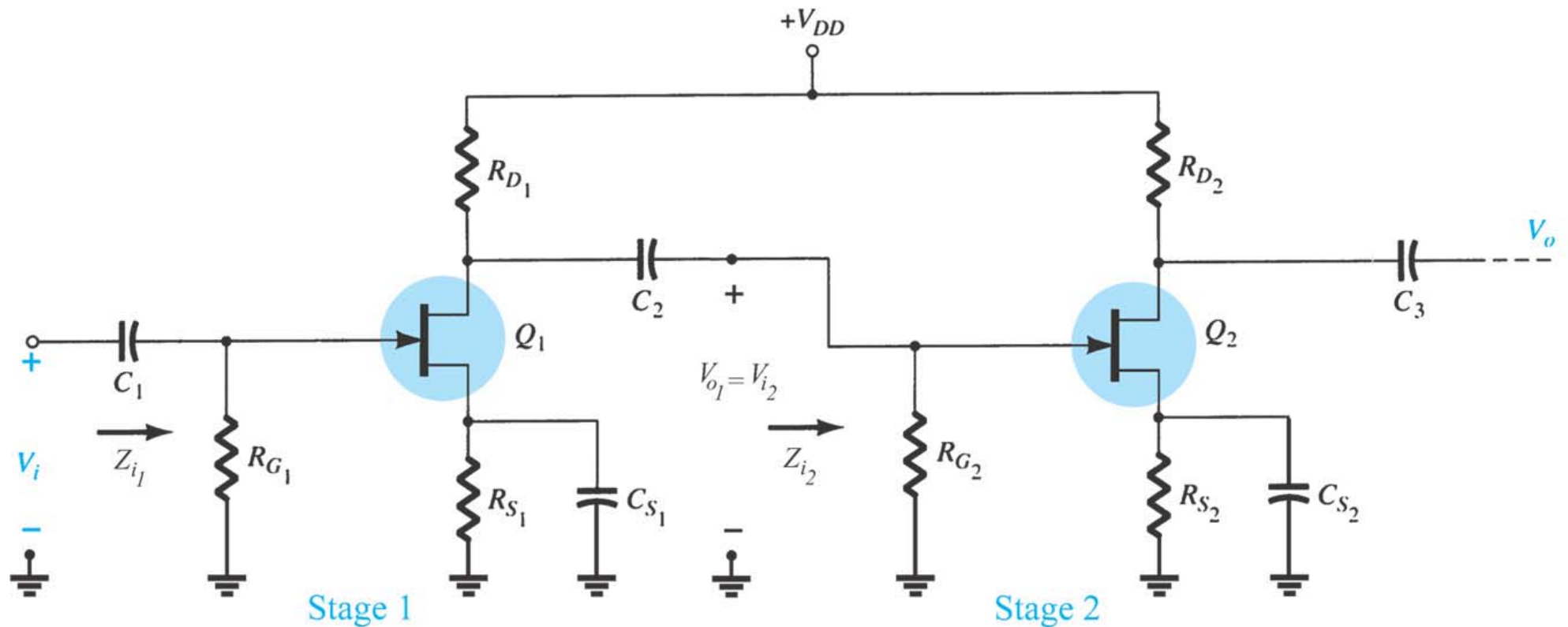8.14 Cascade Configuration

Note: Methods and conclusions are the same with that for BJT amplifiers in 5.16, 5.19.



Summary of FET Amplifiers

- **Comparisons of FETs and BJTs**
 - **Voltage controlled**
 - **High input impedance**
 - **Less sensitive to temperature**
 - **Low power consumption**

- **FET Amplifiers**
 - **Analysis methods are same for FET amplifiers and BJT amplifiers except their specific characteristics and small-signal model**
 - **DC and AC analysis**
 - **cascaded systems**
 - **CS, CG, CD**