

# **Chapter 13**

## **Feedback Circuits**

## 13.1 Feedback Concepts

Feedback types:

### Negative feedback

- The feedback signal is of opposite polarity to the input signal
- Typical application: to improve circuit features

### Positive feedback

- The feedback signal is of same polarity to the input signal
- Typical application: Oscillator circuit


The effects of negative feedback on an amplifier:

### Disadvantage





- Lower gain
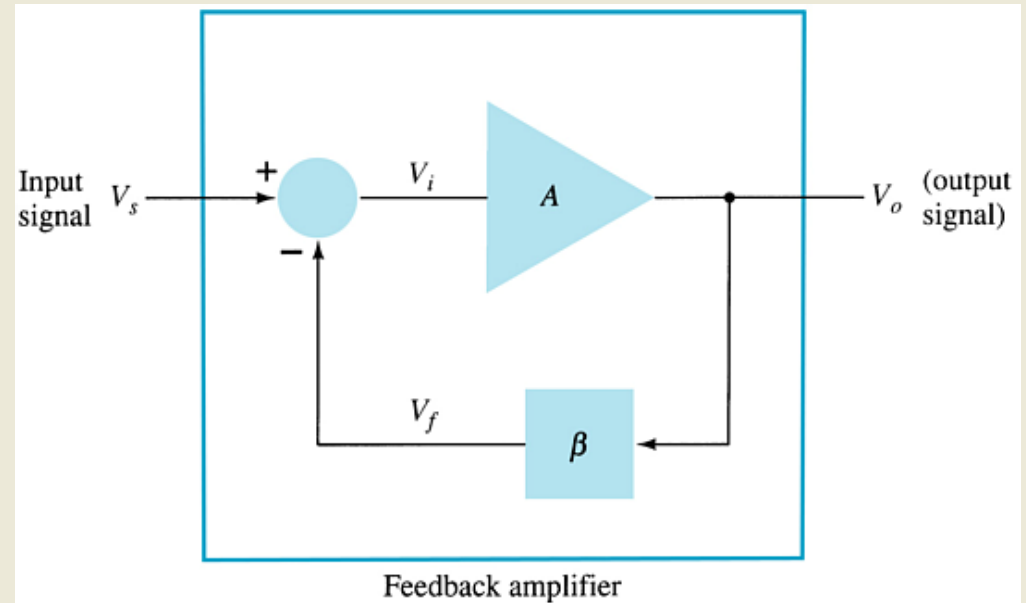
### Advantages

- More stable gain
- Reduced noise
- More linear operation



## 13.2 Feedback Connection Types

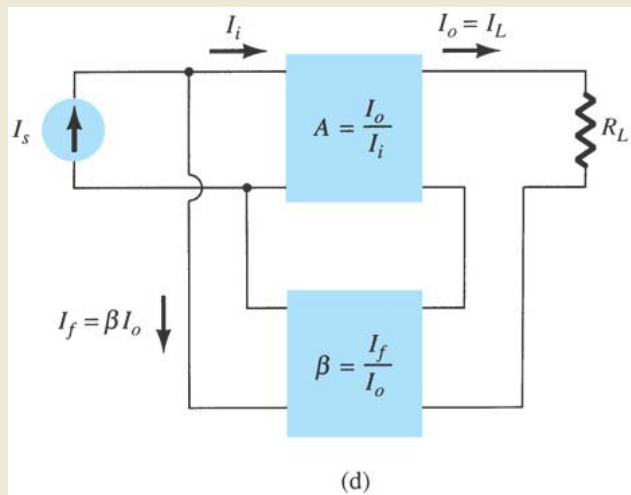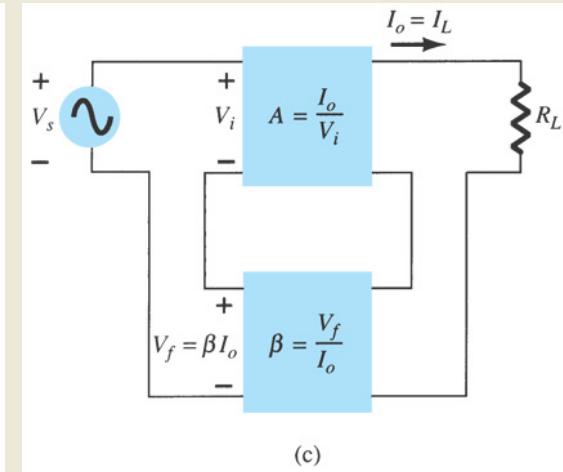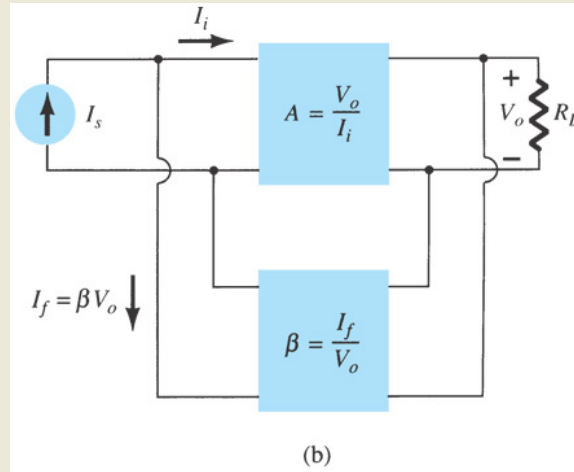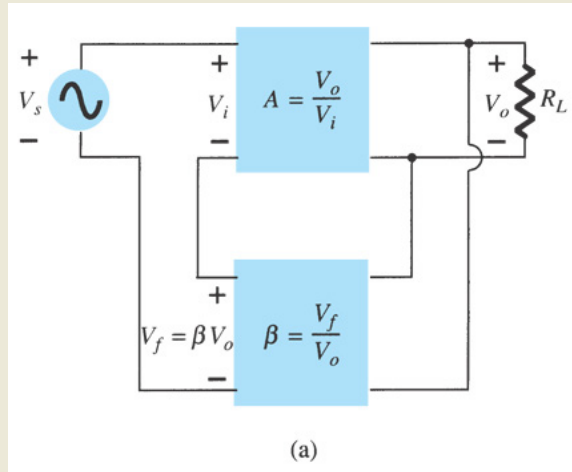

Summary of Gain, Feedback, and Gain with Feedback

		Voltage-Series	Voltage-Shunt	Current-Series	Current
Shunt					
Gain without feedback	$A$	$\frac{V_o}{V_i}$	$\frac{V_o}{I_i}$	$\frac{I_o}{V_i}$	$\frac{I_o}{I_i}$
Feedback	$b$	$\frac{V_f}{V_o}$	$\frac{I_f}{V_o}$	$\frac{V_f}{I_o}$	$\frac{I_f}{I_o}$
	$A_f$	$\frac{V_o}{V_s}$	$\frac{V_o}{I_s}$	$\frac{I_o}{V_s}$	$\frac{I_o}{I_s}$

### Feedback amplifier types:



- (a) voltage-series feedback,  $A_f = V_o / V_s$
- (b) voltage-shunt feedback,  $A_f = V_o / I_s$
- (c) current-series feedback,  $A_f = I_o / V_s$
- (d) current-shunt feedback,  $A_f = I_o / I_s$

### (1) Gain with Feedback:

$$A_f = \frac{A}{1 + \beta A}$$

$$A_f \approx \frac{1}{\beta} \quad \text{when } |\beta A| \gg 1$$

## (2) Input Impedance with Feedback

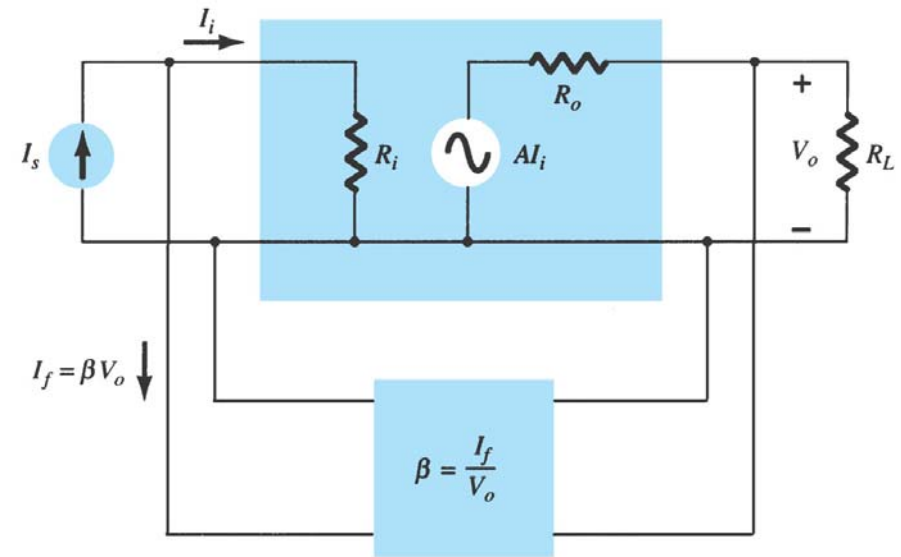
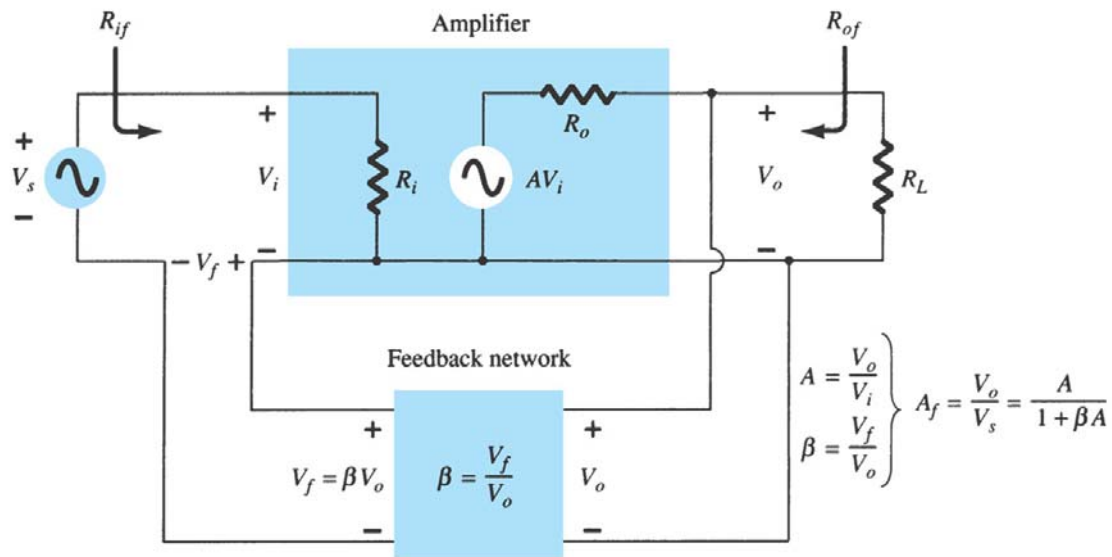


$$Z_{if} = (1 + \beta A)Z_i$$

$$Z_{if} = \frac{Z_i}{1 + \beta A}$$

Effect of Feedback Connection on Input and Output Impedance			
Voltage-Series	Current-Series	Voltage-Shunt	Current-Shunt
$Z_{if} = Z_i (1 + \beta A)$ (increased)	$Z_i (1 + \beta A)$ (increased)	$\frac{Z_i}{1 + \beta A}$ (decreased)	$\frac{Z_i}{1 + \beta A}$ (decreased)
$Z_{of} = \frac{Z_o}{1 + \beta A}$ (decreased)	$Z_o (1 + \beta A)$ (increased)	$\frac{Z_o}{1 + \beta A}$ (decreased)	$Z_o (1 + \beta A)$ (increased)

### (3) Output Impedance with Feedback

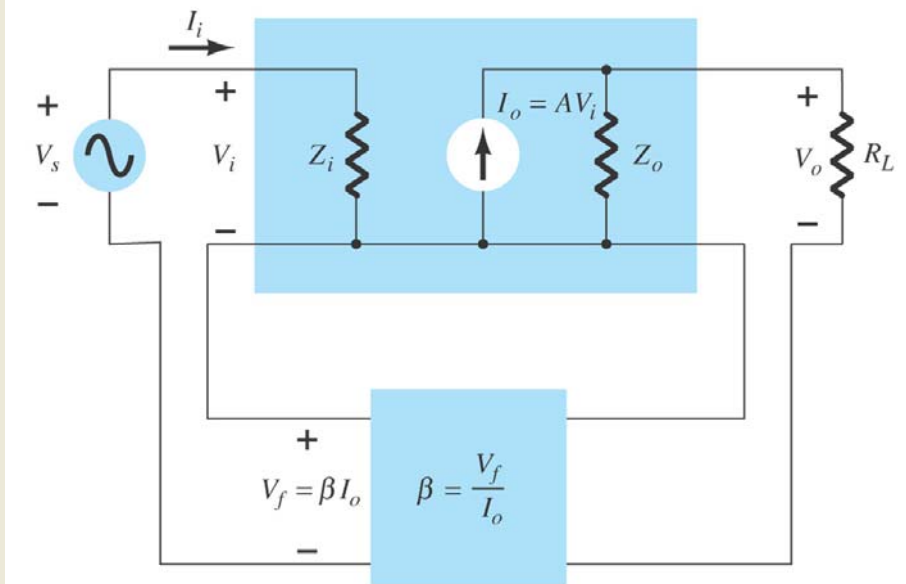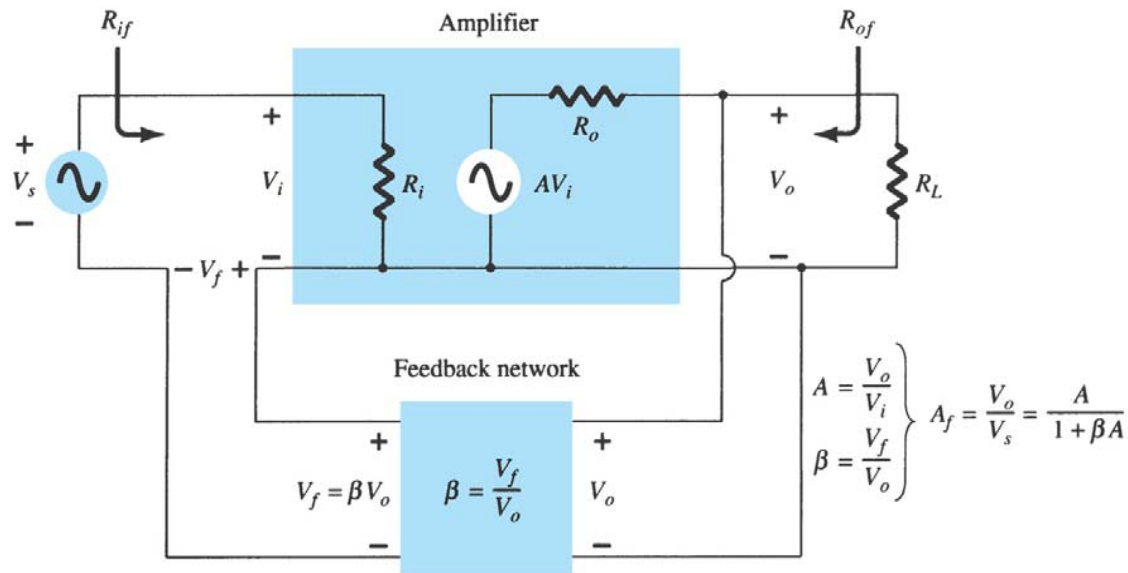

$$Z_{of} = \frac{V}{I} = \frac{Z_o}{(1 + \beta A)}$$

$$Z_{of} = \frac{V}{I} = (1 + \beta A)Z_o$$

Effect of Feedback Connection on Input and Output Impedance			
Voltage-Series	Current-Series	Voltage-Shunt	Current-Shunt
$Z_{if} = Z_i (1 + \beta A)$ (increased)	$Z_i (1 + \beta A)$ (increased)	$\frac{Z_i}{1 + \beta A}$ (decreased)	$\frac{Z_i}{1 + \beta A}$ (decreased)
$Z_{of} = \frac{Z_o}{1 + \beta A}$ (decreased)	$Z_o (1 + \beta A)$ (increased)	$\frac{Z_o}{1 + \beta A}$ (decreased)	$Z_o (1 + \beta A)$ (increased)

## (4) Frequency Distortion with Feedback

- If the feedback network is purely resistive, then the gain with feedback will be less dependent on frequency variations.

$$A_f \approx \frac{1}{\beta} \quad \text{when } |\beta A| \gg 1$$

## (5) Noise and Nonlinear Distortion with Feedback

- The feedback network reduces noise by cancellation. The phase of the feedback signal is often opposite the phase of the input signal.
- Nonlinear distortion is also reduced simply because the gain is reduced. The amplifier is operating in midrange and not at the extremes.


## (6) Bandwidth with Feedback

Feedback increases the bandwidth of an amplifier. The gain-bandwidth product remains the same.

## (7) Gain Stability with Feedback

Gain calculations with feedback are often based on external resistive elements in the circuit. By removing gain calculations from internal variations of  $\beta$  and  $g_m$ , the gain becomes more stable.

$$A_f \approx \frac{1}{\beta} \quad \text{when } |\beta A| \gg 1$$

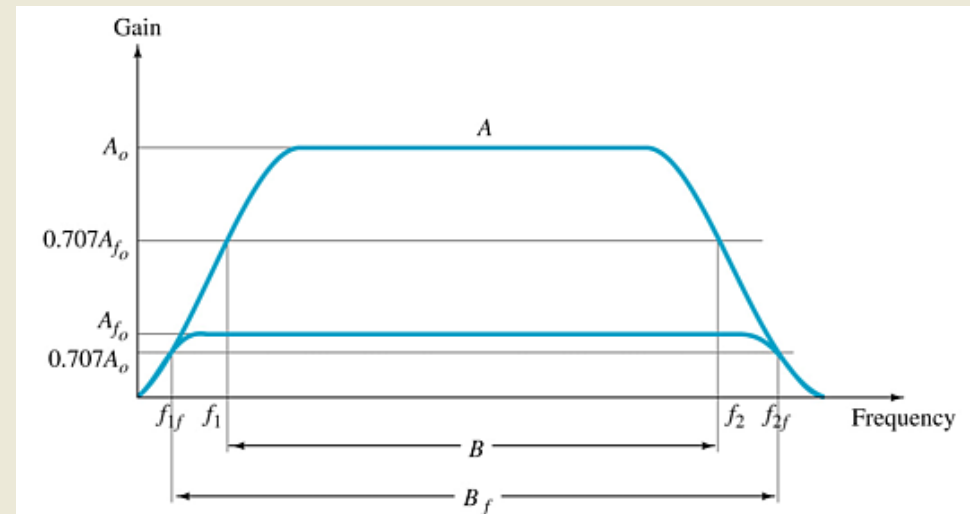

# Summary of Negative Feedback Effects

- Gain
  - Reduced gain, but improve gain stability  $A_f = \frac{A}{1 + \beta A}$
- Input impedance
  - \*\*- series: increase input impedance  $Z_{if} = (1 + \beta A)Z_i$
  - \*\*-shunt: decrease input impedance  $Z_{if} = \frac{Z_i}{1 + \beta A}$
- Output impedance
  - voltage-\*\*: decrease output impedance  $Z_{of} = \frac{Z_o}{(1 + \beta A)}$
  - current-\*\*: increase output impedance  $Z_{of} = (1 + \beta A)Z_o$
- Reduced noise
- More linear operation
- Improve frequency response and increase bandwidth  $B_f = (1 + \beta A)B$

when  $|\beta A| \gg 1$

$$A_f \approx \frac{1}{\beta}$$


$$Z_{if} = \infty$$

$$Z_{if} = 0$$

$$Z_{of} = 0$$

$$Z_{of} = \infty$$

when  $|\beta A| \gg 1$

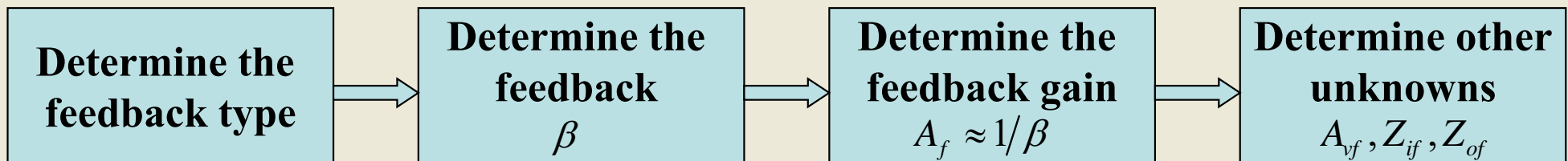

## 13.3 Practical Feedback Circuits


### (a) Voltage-Series Feedback

Open loop:  $A = -g_m(R_D \parallel R_o \parallel (R_1 + R_2))$

$$\beta = \frac{V_f}{V_o} = \frac{R_2}{R_1 + R_2}$$

close loop:  $A_{vf} = A_f = \frac{A}{1 + \beta A}$

If  $|\beta A| \gg 1$   $A_{vf} = A_f \cong \frac{1}{\beta} = \frac{R_1 + R_2}{R_2}$

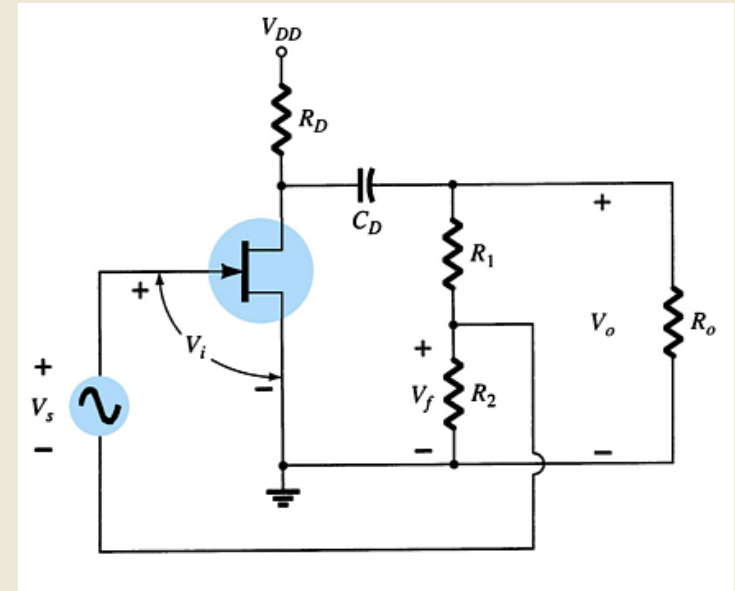

### (b) Voltage-Shunt Feedback



For a voltage-shunt feedback amplifier, the output voltage is fed back in parallel with the input.

$$|\beta A| \gg 1$$

$$\beta = \frac{I_f}{V_o} = -\frac{1}{R_o}$$

$$A_f = \frac{V_o}{I_s} \cong \frac{1}{\beta} = -R_o$$
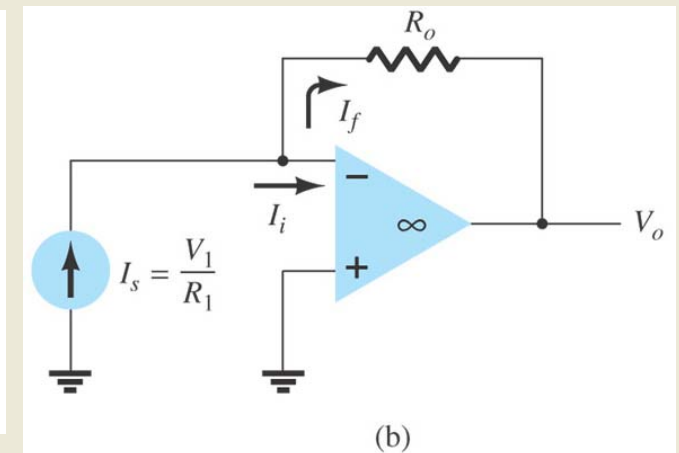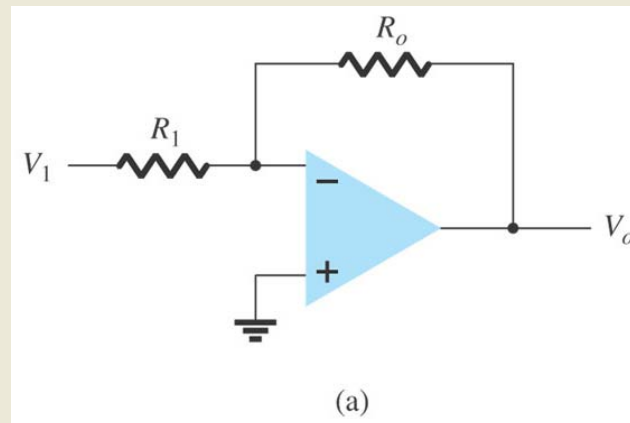
$$A_{vf} = \frac{V_o}{V_i} = \frac{V_o}{I_s R_i} = -\frac{R_o}{R_i}$$





### (c) Current-Series Feedback


Open loop:  $A = \frac{I_o}{V_i} = -\frac{h_{fe}}{h_{ie} + R_E}$        $Z_i = R_B \parallel Z_{ib} = R_B \parallel (h_{ie} + R_E)$

$Z_o = R_C$        $\beta = \frac{V_f}{I_o} = -R_E$

close loop:  $A_f = \frac{I_o}{V_s} = \frac{A}{1 + \beta A}$        $A_{vf} = \frac{I_o R_C}{V_s} = R_C A_f$


$Z_{if} = R_B \parallel (1 + \beta A) Z_{ib}$        $Z_{of} = (1 + \beta A) R_C$

If  $|\beta A| \gg 1$        $A_f = \frac{I_o}{V_s} \cong \frac{1}{\beta} = -\frac{1}{R_E}$        $A_{vf} = \frac{I_o R_C}{V_s} = -\frac{R_C}{R_E}$

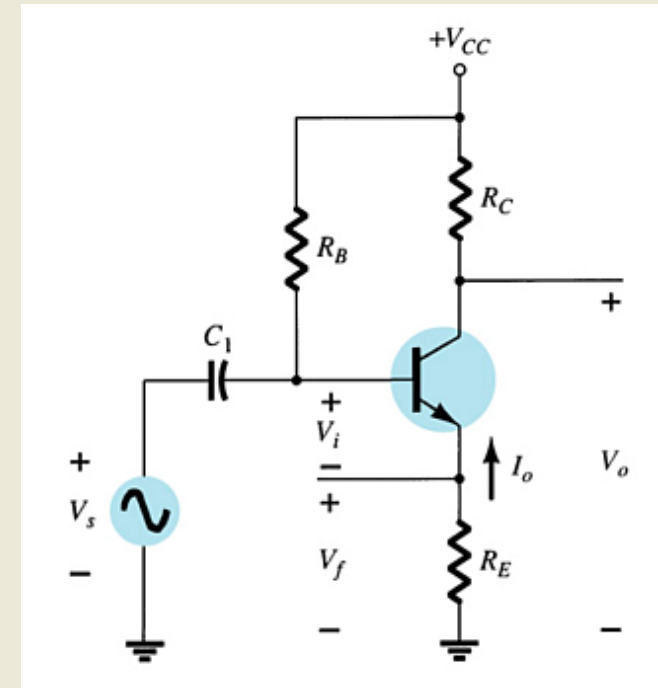

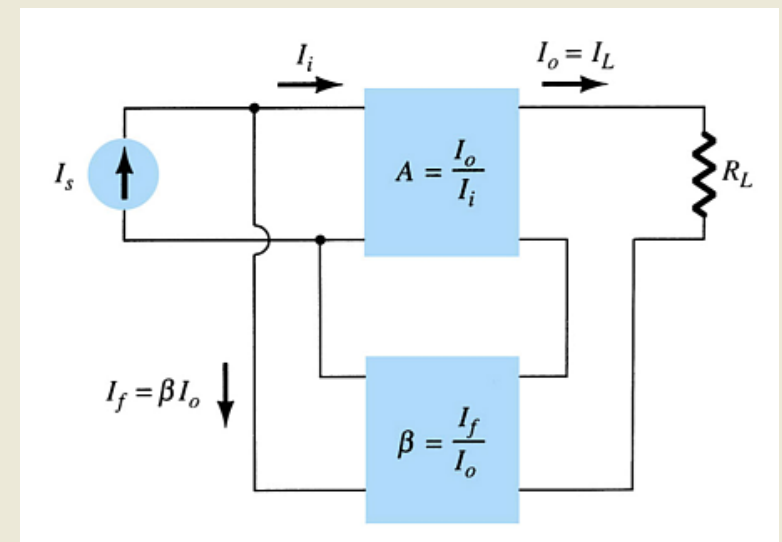
### (d) Current-Shunt Feedback

The feedback gain is given by:  $A_f = \frac{I_o}{I_s}$



## 13.4 Feedback Amplifier-phase and frequency considerations

### Gain and Phase Margins

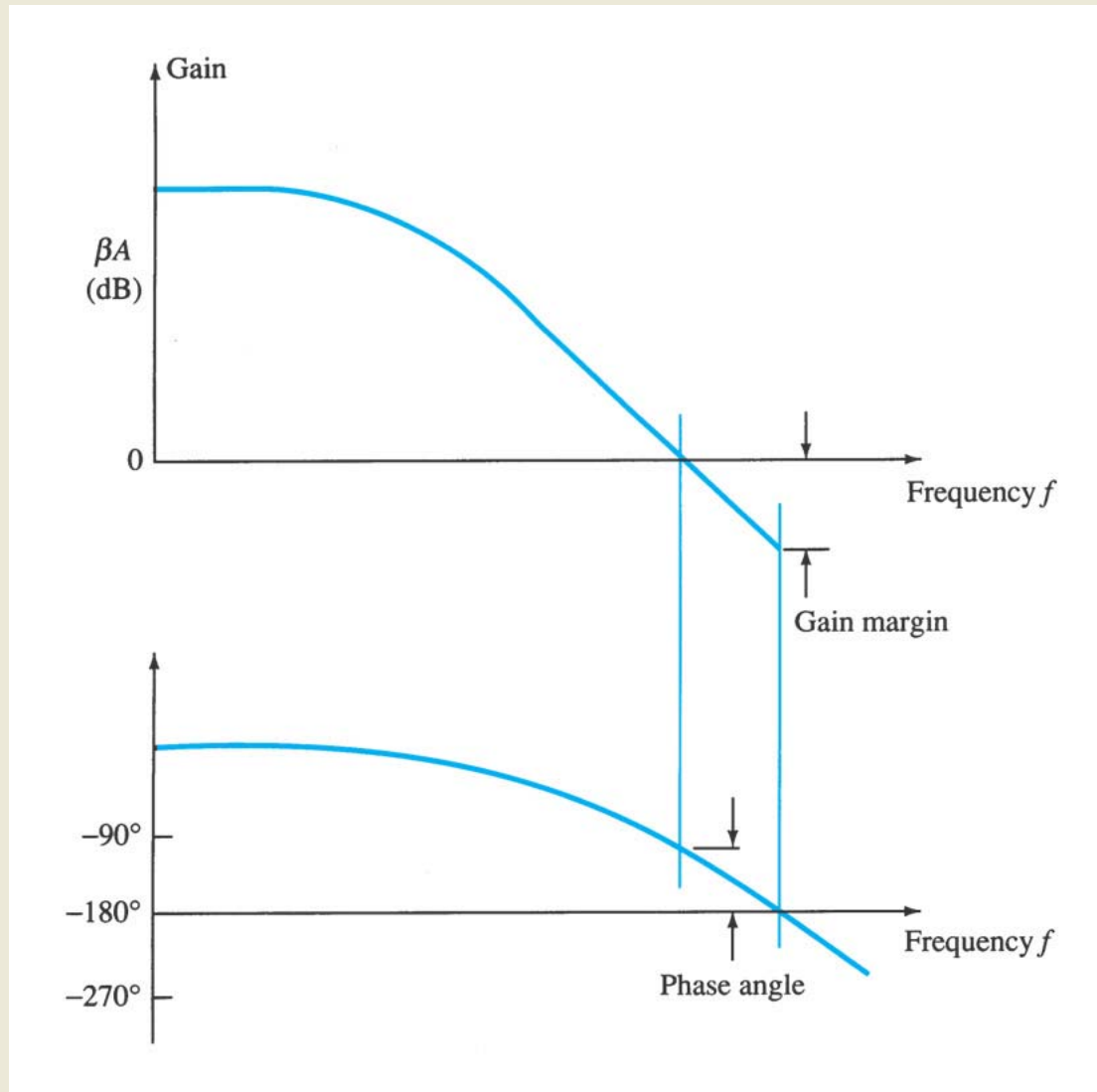

#### Gain margin (GM)

is defined as the negative of the value of  $|\beta A|$  in decibels at the frequency at which the phase angle is  $180^\circ$ .

#### Phase margin (PM)

is defined as the angle of  $180^\circ$  minus the magnitude of the angle at which the value  $|\beta A|$  is unity (0dB)

# Summary of Chapter 13

## Feedback concepts and types of negative feedback

- Find out feedback and determine the type of feedback

## Effects of negative feedback

- Gain
  - Reduced gain, but improve gain stability  $A_f = \frac{A}{1 + \beta A}$
- Input impedance
  - \*- series: increase input impedance  $Z_{if} = (1 + \beta A)Z_i$
  - \*-shunt: decrease input impedance  $Z_{if} = \frac{Z_i}{1 + \beta A}$
- Output impedance
  - voltage-\*: decrease output impedance  $Z_{of} = \frac{Z_o}{(1 + \beta A)}$
  - current-\*: increase output impedance  $Z_{of} = (1 + \beta A)Z_o$
- Reduced noise
- More linear operation
- Improve frequency response and increase bandwidth  $B_f = (1 + \beta A)B$

when  $|\beta A| \gg 1$

$$A_f \approx \frac{1}{\beta}$$

$$Z_{if} = \infty$$

$$Z_{if} = 0$$

$$Z_{of} = 0$$

$$Z_{of} = \infty$$

## Gain and phase margin — stable of a negative feedback amplifier

- To determine whether a negative feedback amplifier is stable.