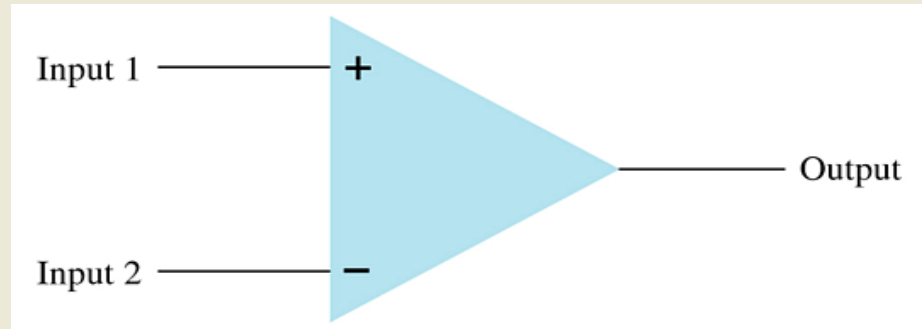


10.1 Introduction

Construction of op-amp



Note the op-amp has two inputs and one output.





Characteristics of op-amp

- amplifying the differential signal while rejecting the common signal at the two inputs
- very high gain differential amplifier
- high input impedance (typically a few meg-Ohms)
- low output impedance (less than 100 Ω).

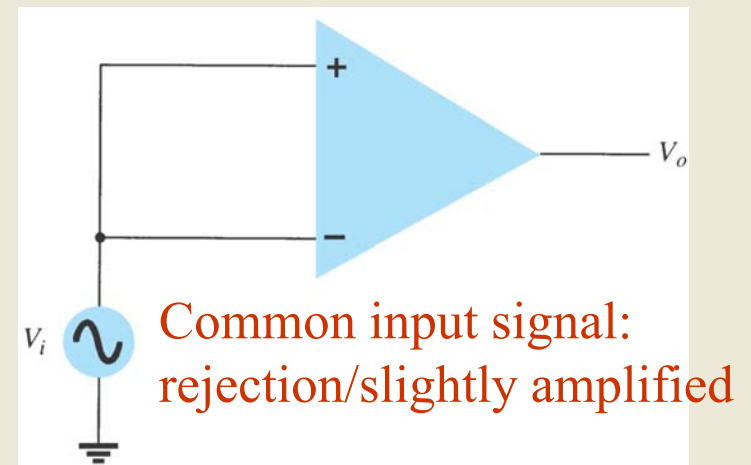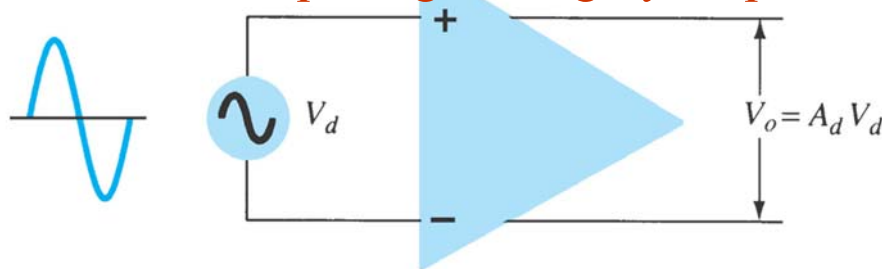Differential input signal: highly amplified



10.2 Differential Amplifier Circuit

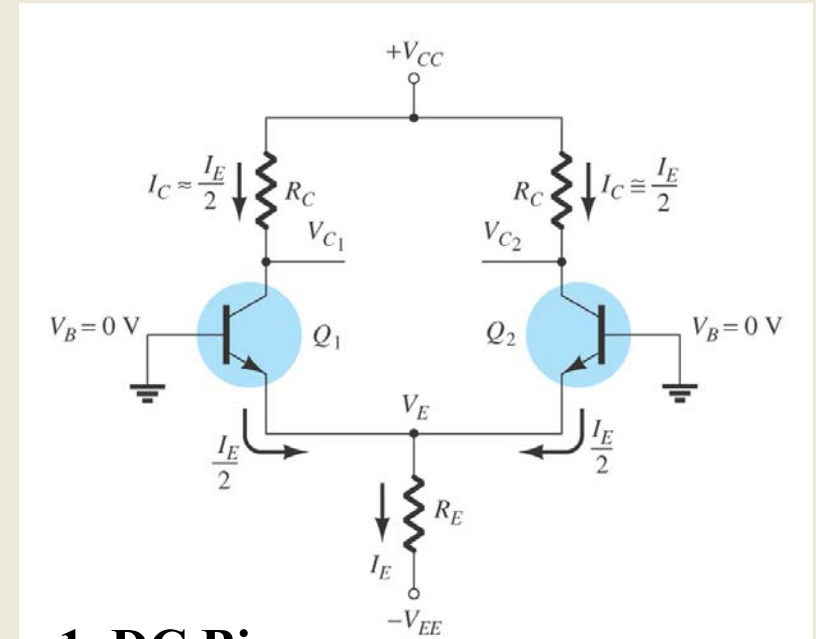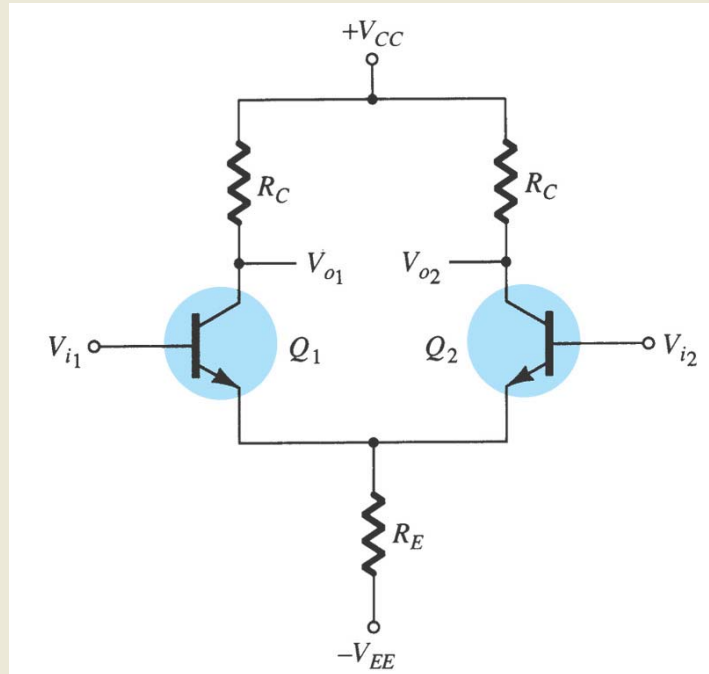

1. DC Bias

$$V_E = -0.7V \quad I_E = \frac{-0.7V - (-V_{EE})}{R_E}$$

$$I_{C1} = I_{C2} = \frac{I_{EE}}{2} \quad V_{C1} = V_{C2} = V_{CC} - \frac{I_E}{2} R_C$$

2. AC operation

- Differential-mode operation** $V_o = A_d V_d$

double ended with input $\frac{V_d}{2}, -\frac{V_d}{2}$

- Common-mode operation** $V_o = A_c V_c$

double ended with input V_c, V_c

- (1) A fundamental building block of analog ICs.
- (2) Two possible inputs and two possible outputs
- (3) Identical transistor characteristics of the differential-pair
- (4) Amplifying differential-mode input voltage $V_d = V_{i1} - V_{i2}$, rejecting differential-mode input voltage $V_c = (V_{i1} + V_{i2})/2$
- (5) High gain, high input impedance, and low output impedance

Differential Inputs $V_d = V_{i1} - V_{i2}$


Common Inputs $V_c = \frac{1}{2}(V_{i1} + V_{i2})$



$$V_{i1} = V_c + \frac{1}{2} V_d$$

$$V_{i2} = V_c - \frac{1}{2} V_d$$

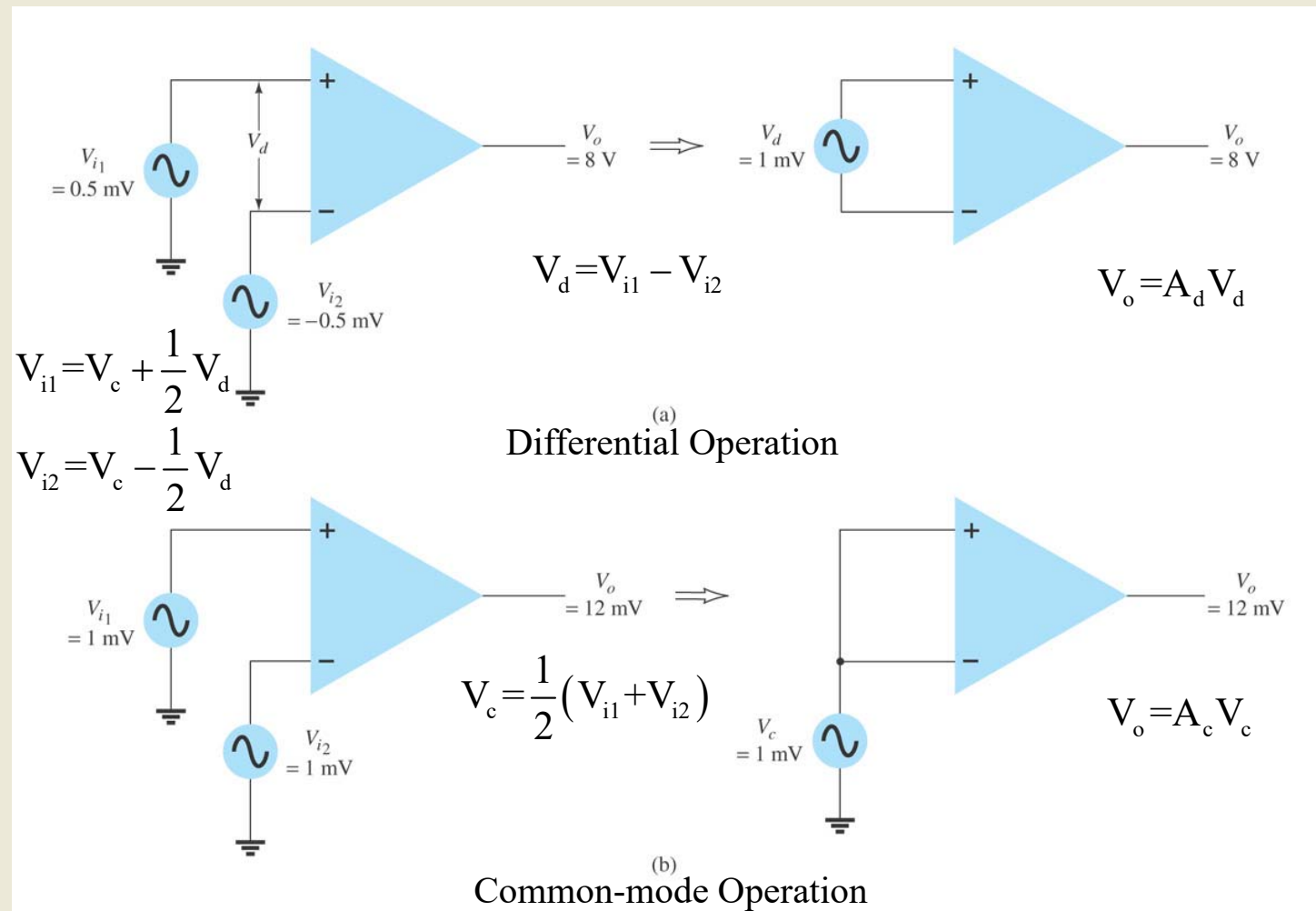10.3 Differential And Common-mode Operation



CMRR:


Any signal that is common to both inputs will be cancelled. A measure of the ability to cancel out common signals is called **CMRR (common-mode rejection ratio)**.

$$\text{CMRR} = \frac{A_d}{A_c}$$

$$\text{CMRR (log)} = 20 \log_{10} \frac{A_d}{A_c} = A_d (\text{dB}) - A_c (\text{dB})$$


Use of Constant-Current Source

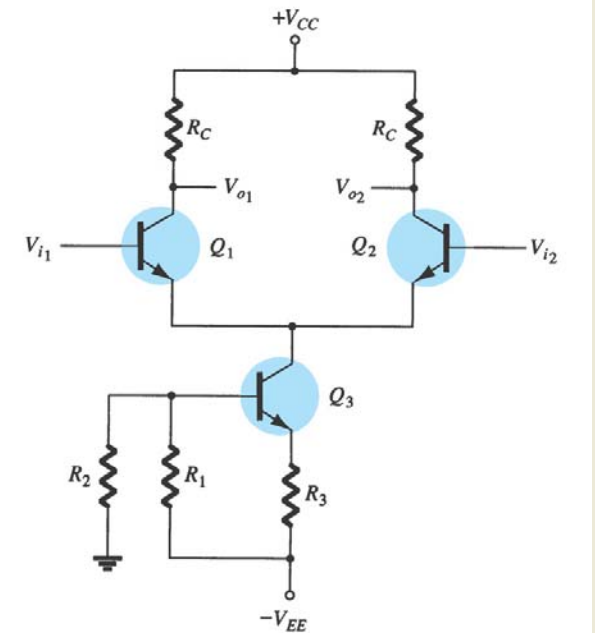- To provide operating point as well as increasing common-mode rejection ability (provide a large value of the emitter resistance to reduce A_c).
- To be used as active load to improve the differential gain




Use of BiFET, BiMOS, and CMOS Differential Amplifier Circuits

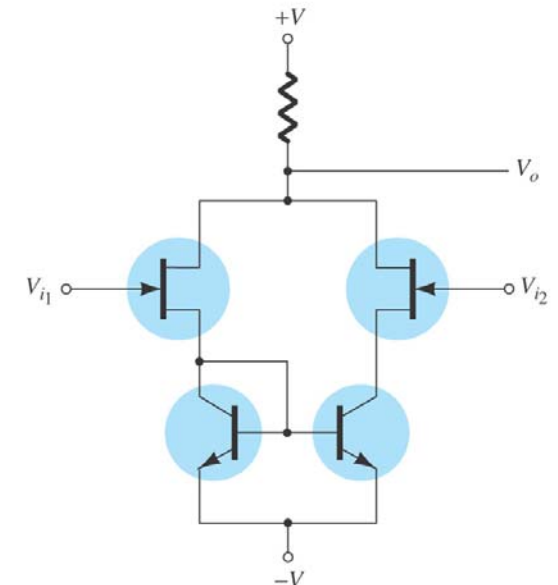
- BiFET: a differential amplifier by both BJT and JFET
- BiMOS: a differential amplifier by both BJT and MOSFET
 - Combine BJT and MOS transistors on the same semiconductor chip
 - The advantages of the MOSFET high input impedance and the BJT high gain can be combined and utilized in the same circuit
- CMOS: a differential amplifier by complementary type MOSFET
 - Low power dissipation




10.5 Op-Amp Basics

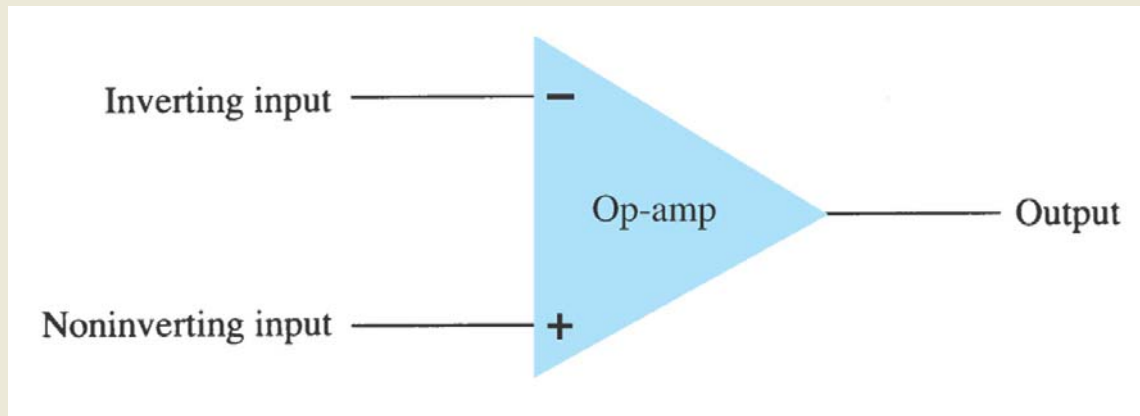

Ideal

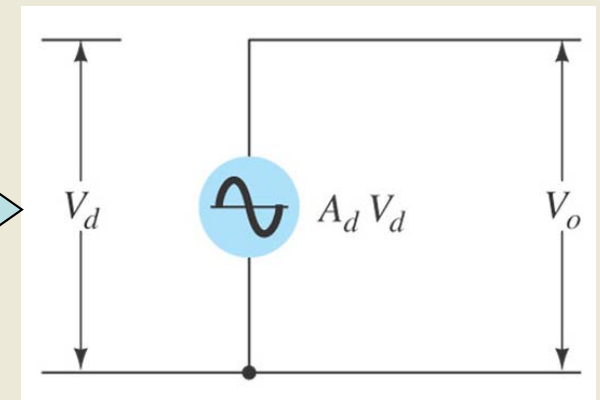

Practical

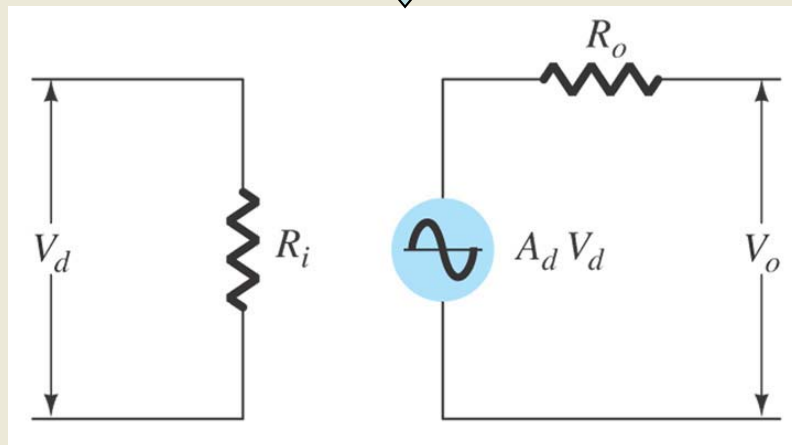

Ideal features of op-amp:

- $A_d = \infty, A_c = 0$
- $R_i = \infty$
- $R_o = 0$


$$V_d = \frac{V_o}{A_d} \Rightarrow \text{Virtual Short: } V_d = 0$$

$$I_d = \frac{V_d}{R_i} \Rightarrow \text{Virtual Open: } I_d = 0$$

Practical features of op-amp:

- very high gain A_d for differential input V_d
- high input impedance R_i (typically a few meg-Ohms)
- low output impedance R_o (less than 100 Ω).


(1) Inverting constant gain amplifier

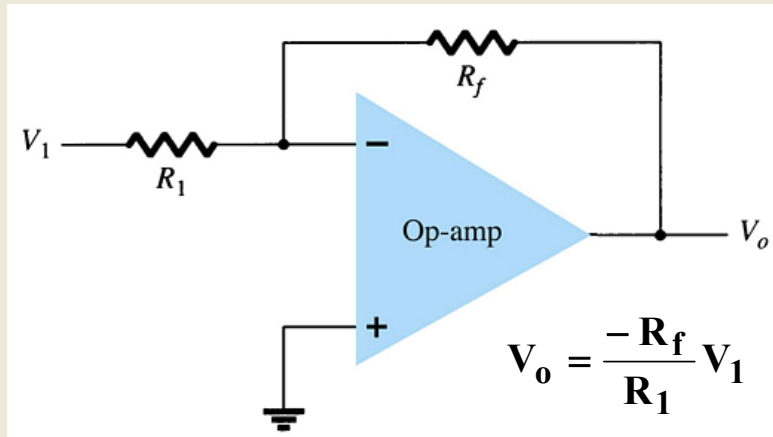


- The signal input is applied to the **inverting (-) input**
- The **non-inverting input (+)** is grounded
- The resistor R_f is the **feedback resistor**.

The *non-inverting input* pin is at ground.
The *inverting input* pin is also at 0V for an AC signal due to virtual short concept.
The *inverting input* is at **virtual ground**.

(2) Noninverting constant gain amplifier

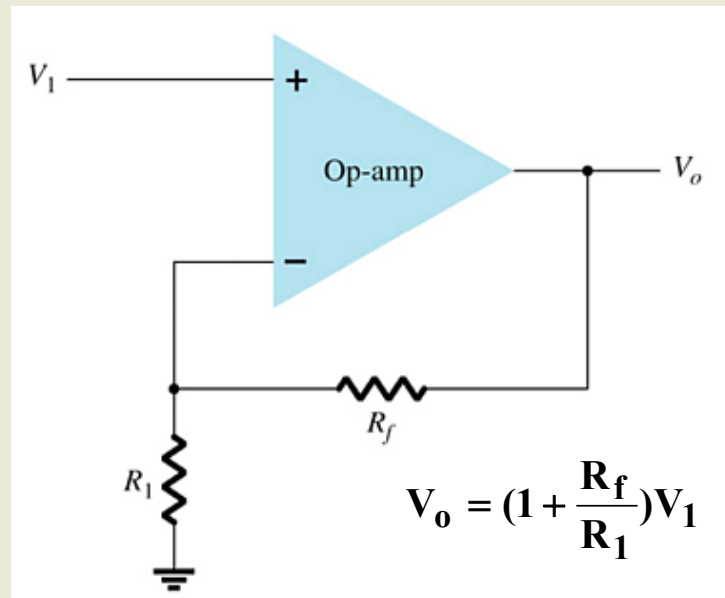

(3) Unity follower → **Voltage buffer**

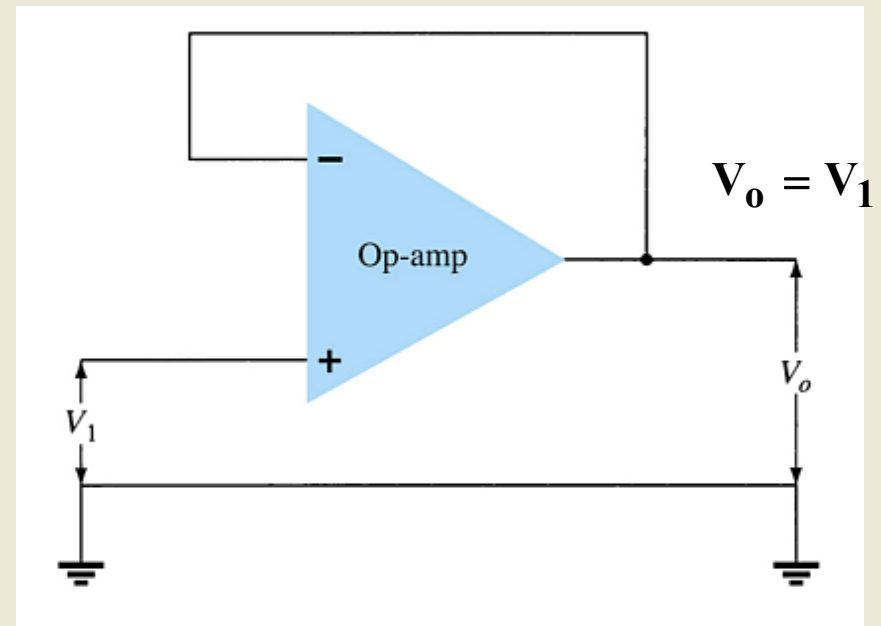

10.6 Op-Amp Specifications—DC Offset Parameters

Even when the input voltage is zero, there will be an output called **offset**. The following can cause this offset:

- Input offset voltage (V_{IO})
- Input offset current (I_{IO})
- Total offset voltage may due to both input offset voltage *and* input offset current

$$V_o(\text{offset}) = V_o(\text{offset due to } V_{IO}) + V_o(\text{offset due to } I_{IO})$$

- Input bias current (I_{IB})

$$I_{IB}^- = I_{IB} - \frac{I_{IO}}{2} \quad I_{IB}^+ = I_{IB} + \frac{I_{IO}}{2} \quad I_{IB} = \frac{I_{IB}^- + I_{IB}^+}{2}$$

In experiments and actual applications, adjusting circuits for zero-input zero-output is employed.

10.7 Op-Amp Specifications—Frequency Parameters

An op-amp is a wide-bandwidth amplifier. The following affect the bandwidth of the op-amp:


- Gain
- Slew rate
- The plot shown is for an open loop gain (A_{OL} or A_{VD}).
- The op-amp's high frequency response is limited by internal circuitry.
- In the open loop, the op-amp has a narrow bandwidth.
- The bandwidth widens in closed-loop operation, but then the gain is lower.

$$f = f_1, \quad A_{VD} = 1$$

$$f = f_c, \quad A_{VD} = 0.707A_{VD0}$$

$$f_1 = f_c A_{VD0}$$

f_1 is called the gain-bandwidth

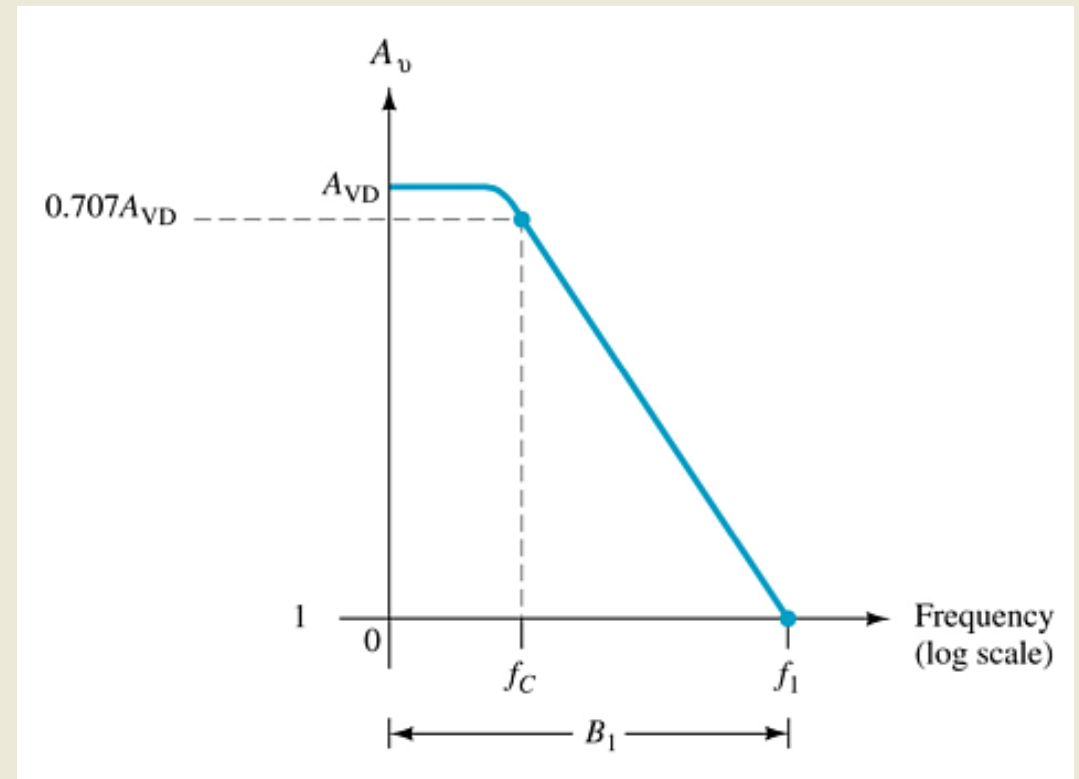

Summary of Chapter 10

- **Characteristics of Differential Amplifier**
 - **Differential mode operation**
 - **Common mode operation**
 - **CMRR**
- **Characteristics of Op-Amp.**
 - **Ideal assumptions (Virtual short and Virtual open)**
 - **Practical**
- **Linear applications of Op-Amp**
 - **Inverting and noninverting amplifier**
 - **Unity follower**