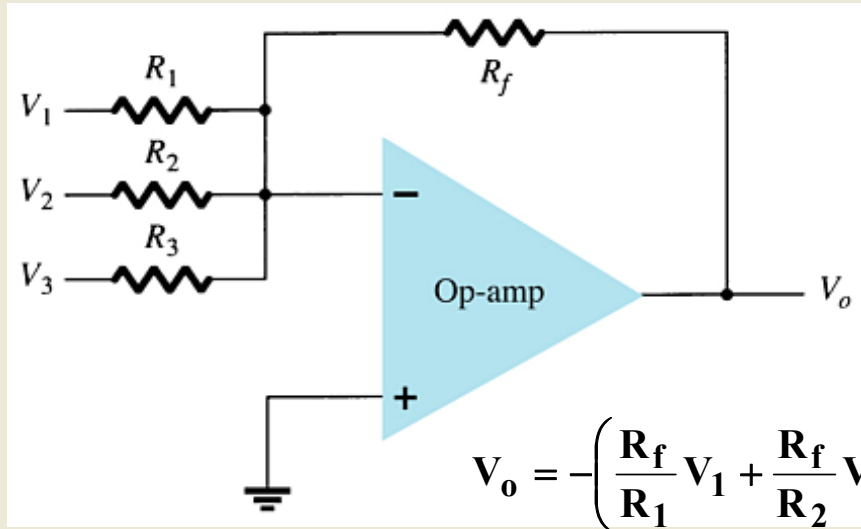


# **Chapter 11**

## **Op-Amp Applications**


# 11.1 Operation Circuits

## (1) Summing amplifier




$$V_o = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3\right)$$

## (2) Voltage Subtraction

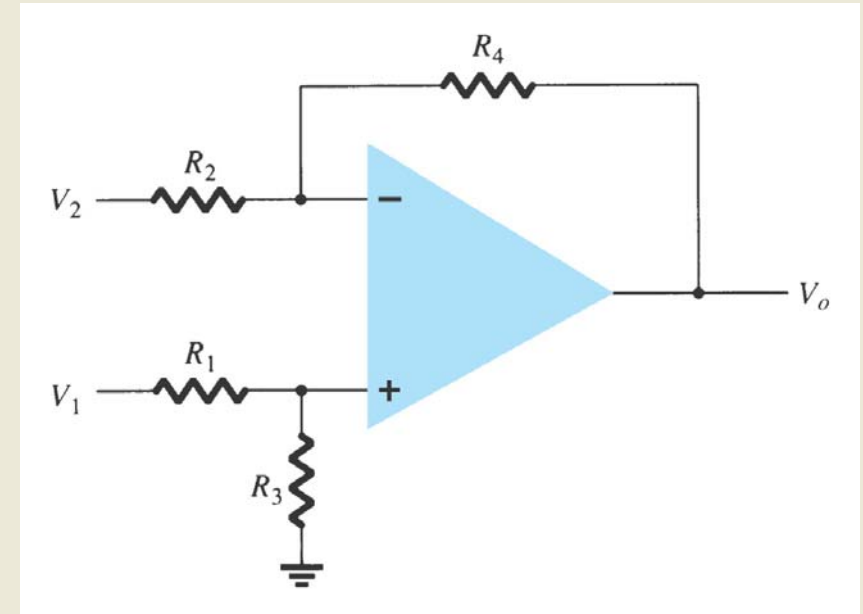

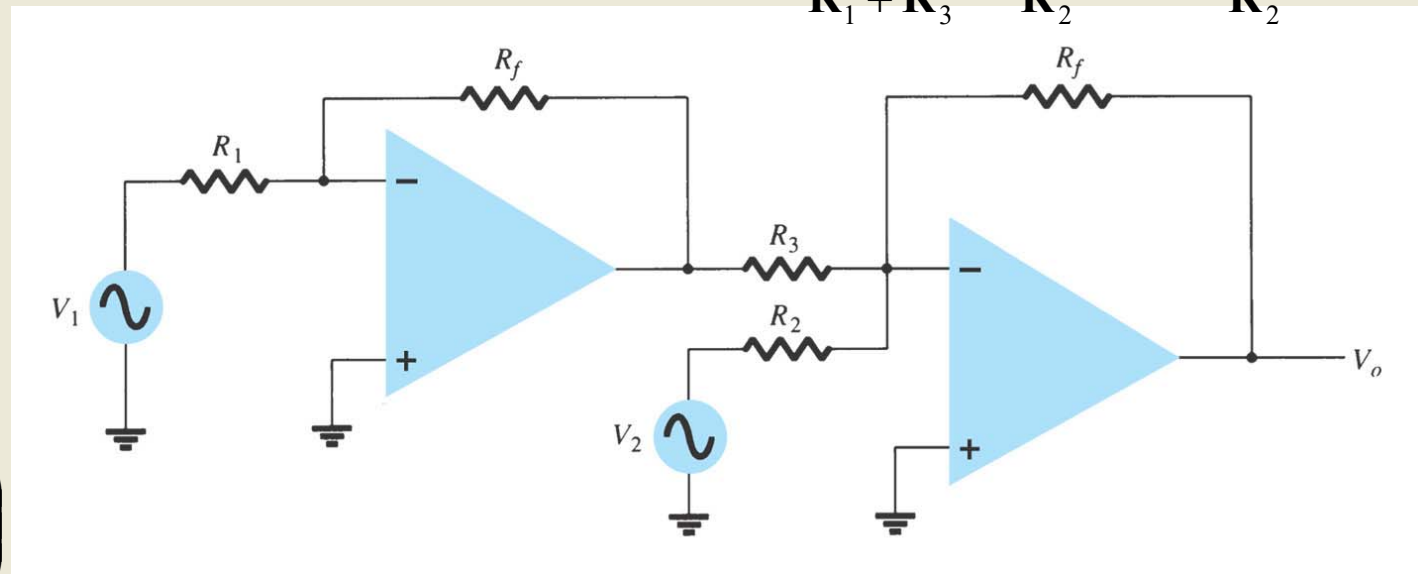
$$V_o = \frac{R_3}{R_1 + R_3} \frac{R_2 + R_4}{R_2} V_1 - \frac{R_4}{R_2} V_2$$




$$V_o = -\left(\frac{R_f}{R_2} V_2 - \frac{R_f}{R_3} \frac{R_f}{R_1} V_1\right)$$

### (3) Integrator

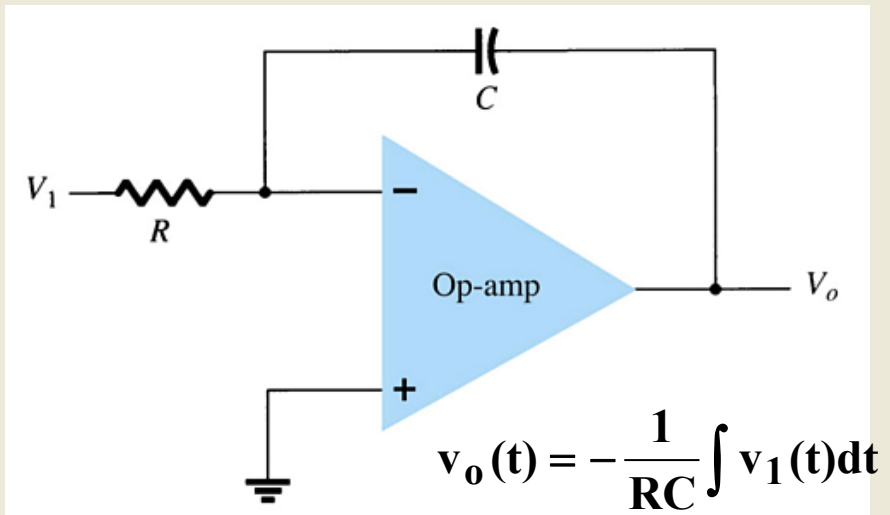


### (4) Differentiator

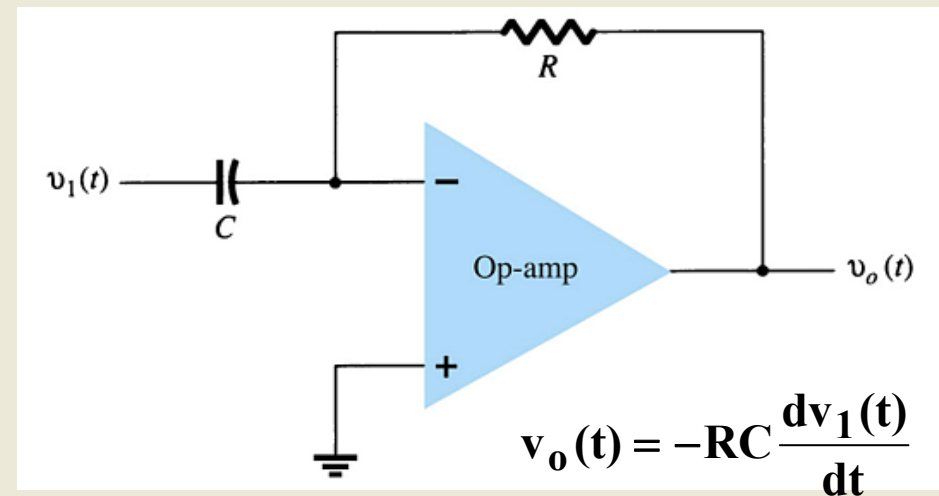


## 11.2 Active Filter


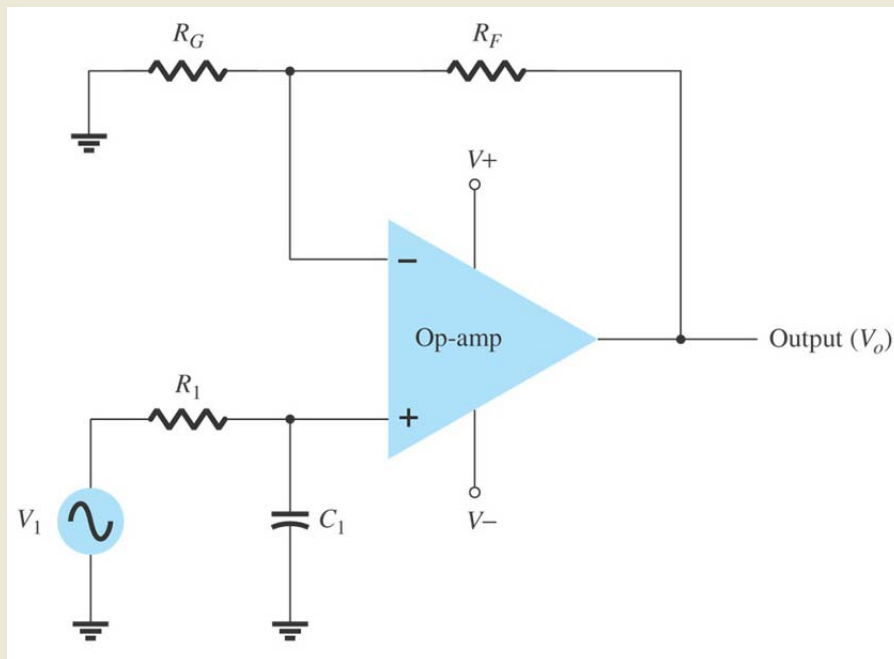
### (1) First-order low-pass active filter


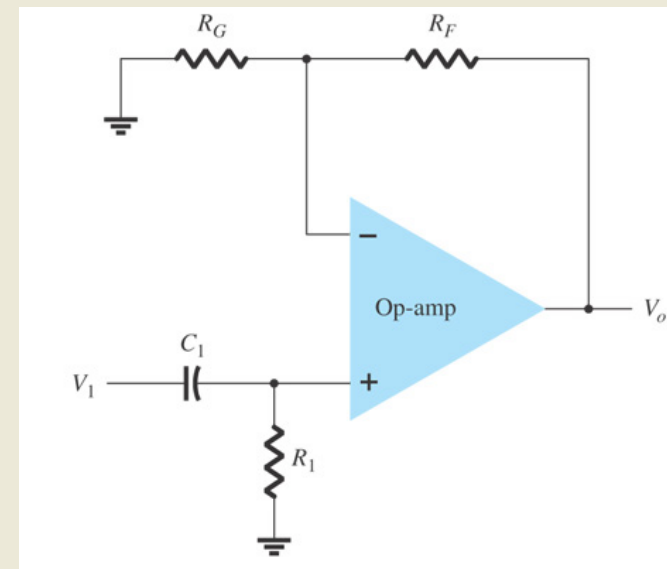
### (2) First-order high-pass active filter



## 11.3 Comparator Circuit

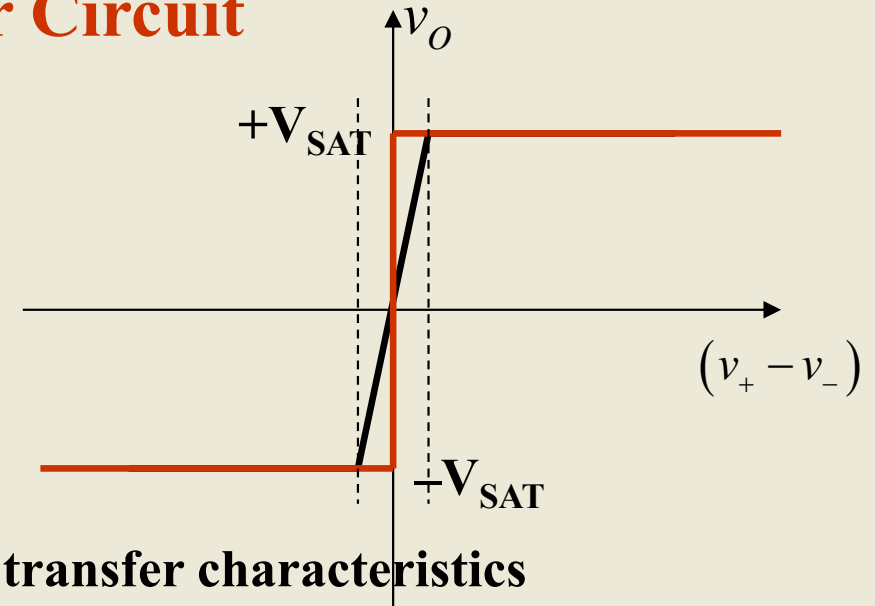
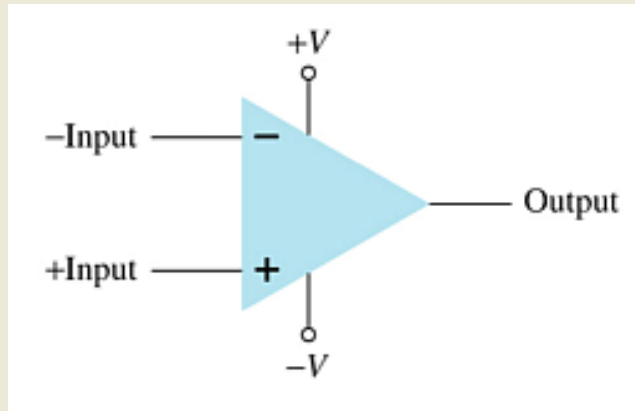


### Open-loop Comparators and voltage transfer characteristics

The operation is a basic comparison. The output swings between its maximum and minimum voltage, depending upon whether one input ( $V_i$ ) is greater or less than the other ( $V_{ref}$ ).



For a **noninverting op-amp comparator**:

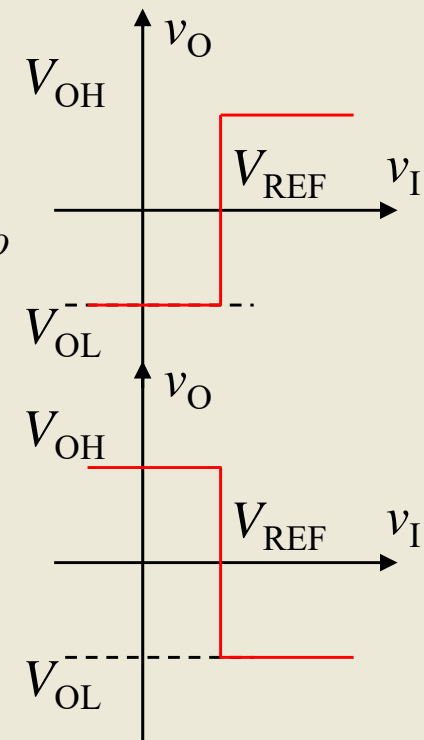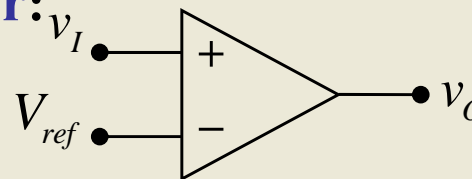- $V_o = +V_{SAT}$  when  $V_i > V_{ref}$
- $V_o = -V_{SAT}$  when  $V_i < V_{ref}$



For a **inverting op-amp comparator**:

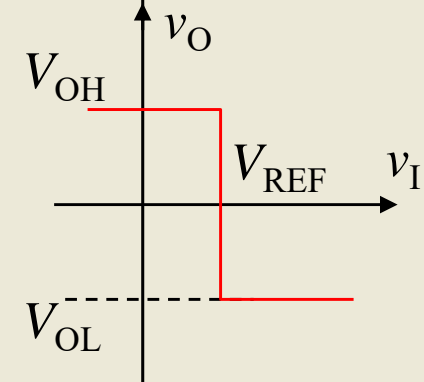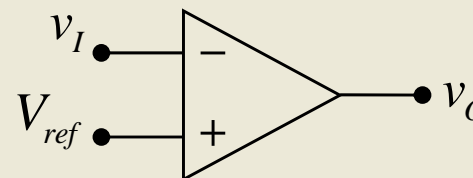- $V_o = -V_{SAT}$  when  $V_i > V_{ref}$
- $V_o = +V_{SAT}$  when  $V_i < V_{ref}$



# Use of Op-Amp as Comparator

## Example:



- $V_{\text{ref}}$  in this circuit is +6V (from voltage divider)
- $+V_{\text{SAT}} = +V$ , or +12V
- $-V_{\text{SAT}} = -V$  or -12V

When  $V_i > +6\text{V}$  the output swings to +12V and the LED goes on.

When  $V_i < +6\text{V}$  the output is at -12V and the LED goes off.

When  $V_i < +6\text{V}$  the output swings to +12V and the LED goes on.

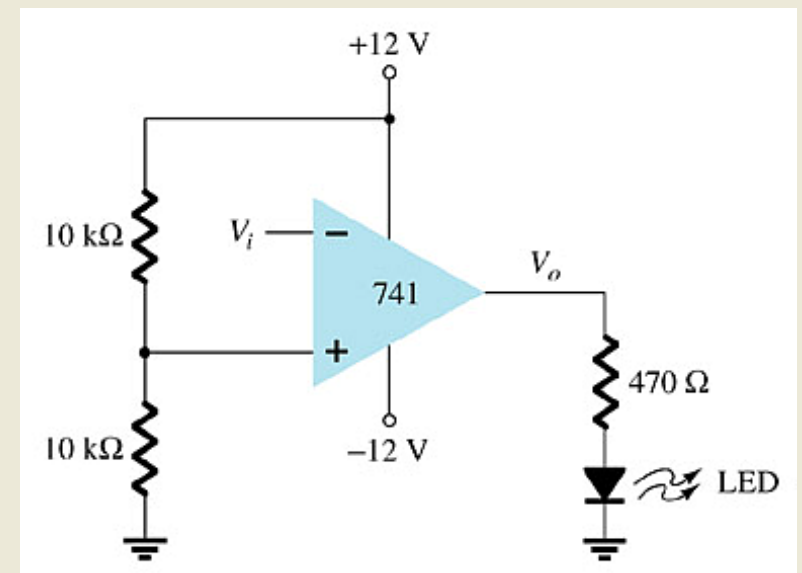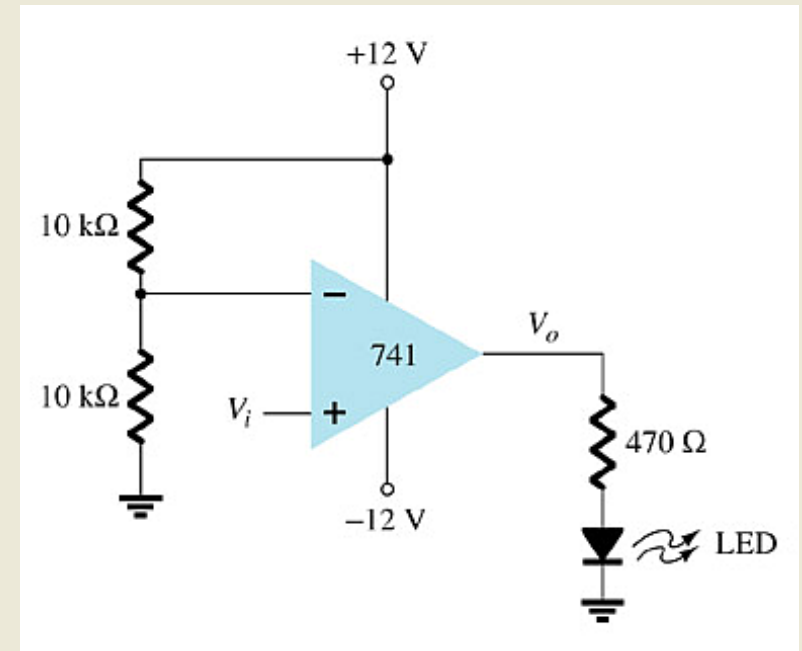When  $V_i > +6\text{V}$  the output is at -12V and the LED goes off.



# Comparator ICs



## Advantages:

- Faster switching
- Built-in noise immunity
- Outputs capable of directly driving loads

## Example of Comparator ICs


- 311
- 339

## Voltage transfer characteristic

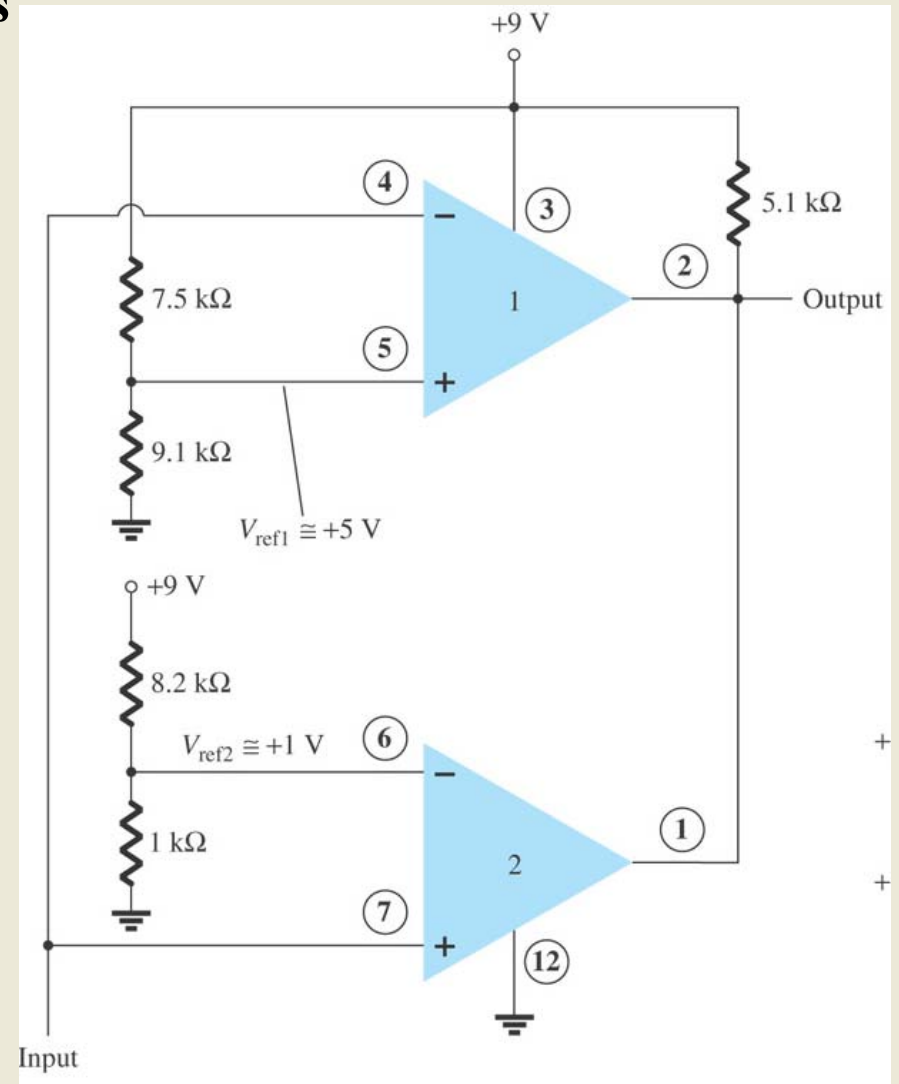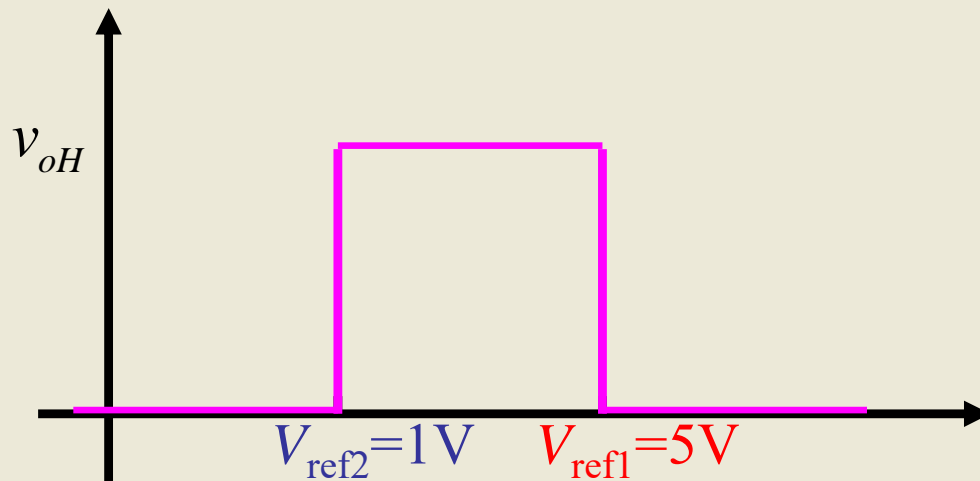

## 11.4 Schmitt Trigger

### Basic inverting Schmitt Trigger

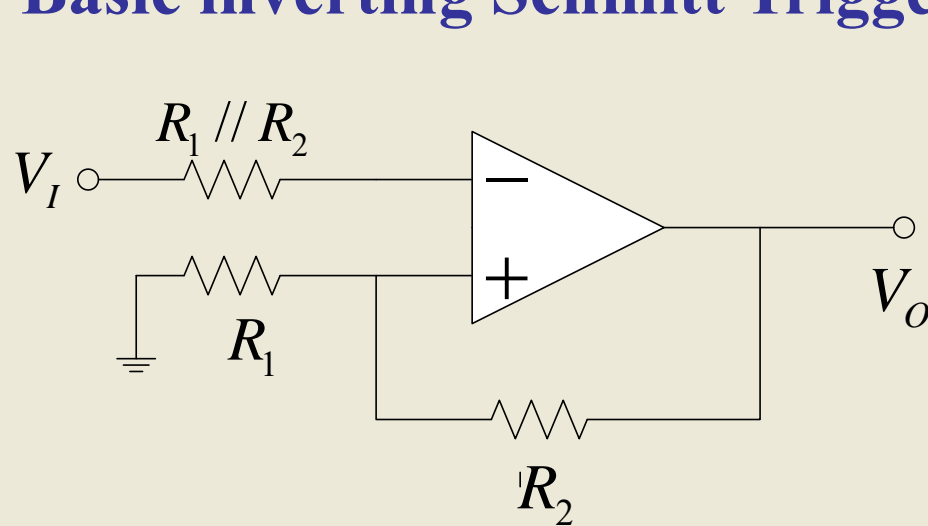

$$v_- = v_I \quad v_+ = \frac{R_1}{R_1 + R_2} v_O$$

(1) when  $v_O = V_{OH}$ , high state

$$v_+ = \frac{R_1}{R_1 + R_2} V_{OH}$$

**crossover occurs when  $v_I = v_+$**

$$V_{TH} = \frac{R_1}{R_1 + R_2} V_{OH}$$


(2) when  $v_O = V_{OL}$ , low state

$$v_+ = \frac{R_1}{R_1 + R_2} V_{OL}$$


**crossover occurs when  $v_I = v_+$**

$$V_{TL} = \frac{R_1}{R_1 + R_2} V_{OL}$$


voltage transfer characteristics

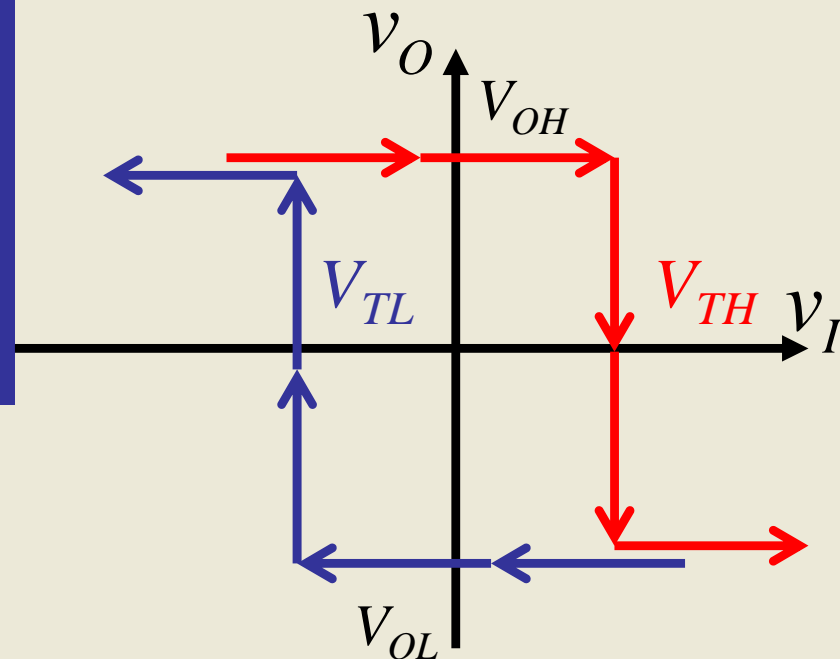

# Noninverting Schmitt Trigger

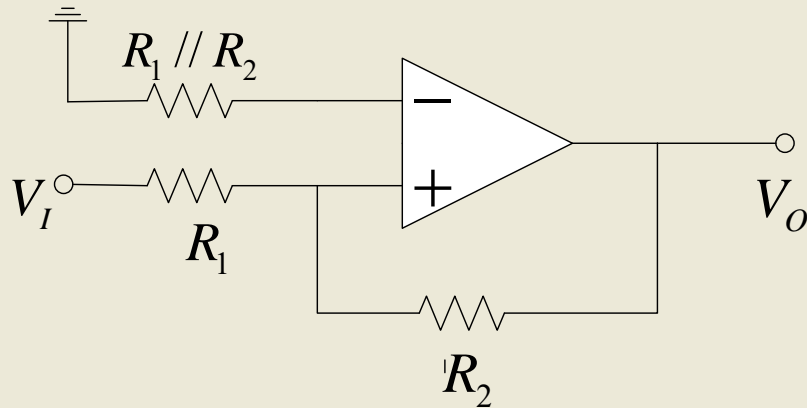

voltage transfer characteristics

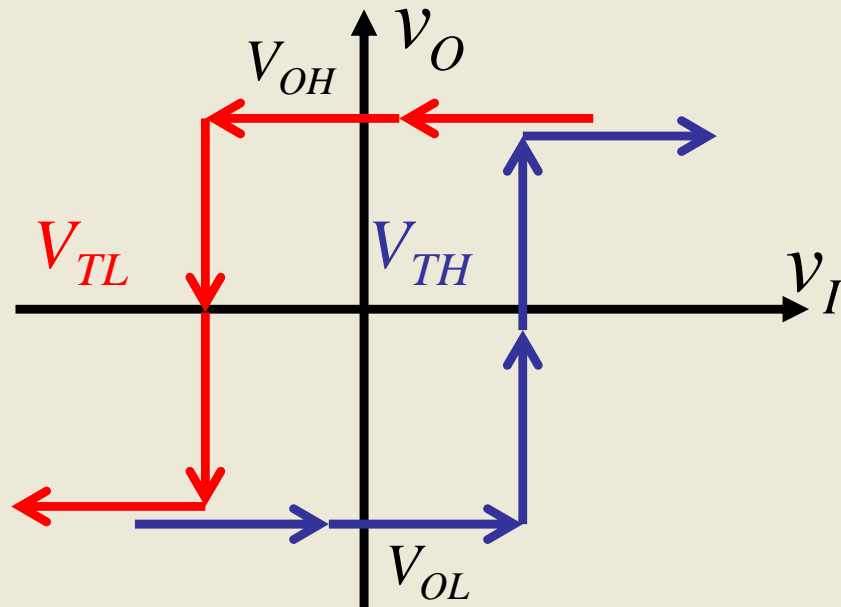

## Additional Schmitt Trigger Configurations

- With output limiters
- With applied reference voltages

$$v_- = 0 \quad v_+ = \frac{R_2}{R_1 + R_2} v_I + \frac{R_1}{R_1 + R_2} v_O$$

(1) when  $v_O = V_{OH}$ , high state

$$v_+ = \frac{R_2}{R_1 + R_2} v_I + \frac{R_1}{R_1 + R_2} V_{OH}$$

**crossover occurs when  $v_+ = 0$**

$$V_I = V_{TL} = -\frac{R_1}{R_2} V_{OH}$$

(2) when  $v_O = V_{OL}$ , low state

$$v_+ = \frac{R_2}{R_1 + R_2} v_I + \frac{R_1}{R_1 + R_2} V_{OL}$$

**crossover occurs when  $v_+ = 0$**

$$V_I = V_{TH} = -\frac{R_1}{R_2} V_{OL}$$



## Summary of Chapter 11

- **Linear Applications**
  - **11.1 Operational Circuits**
  - **11.2 Active Filter**
- **Nonlinear Applications**
  - **11.3 Comparator**
  - **11.4 Schmitt Trigger**